

Name _____

Units?
Units?


Phys 2020
Quiz #2 — Fall 2002

1. When a potential difference of 50.0 V is applied to the plates of a capacitor, it is found that a charge of $7.0 \mu\text{C}$ is stored.

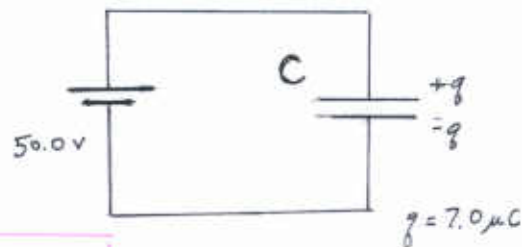a) What is the value of the capacitance?

Use $q = CV$, then:

$$C = \frac{q}{V} = \frac{(7.0 \times 10^{-6} \text{ C})}{50.0 \text{ V}} = \boxed{1.4 \times 10^{-7} \text{ F} = 0.14 \mu\text{F}}$$



b) How much energy is stored in the capacitor under these conditions?

Use $(\text{Energy}) = \frac{1}{2} CV^2$, then:


$$\text{Energy} = \frac{1}{2} (1.4 \times 10^{-7} \text{ F}) (50.0 \text{ V})^2 = \boxed{1.75 \times 10^{-4} \text{ J}}$$

c) If all of this energy is delivered to a strobe lamp in 0.350 ms, what is the (average) power delivered to the lamp?

Use $\text{Power} = \frac{\text{Energy del'd}}{\Delta t}$, then

$$P = \frac{1.75 \times 10^{-4} \text{ J}}{(0.350 \times 10^{-3} \text{ s})} = \boxed{0.50 \text{ W}}$$

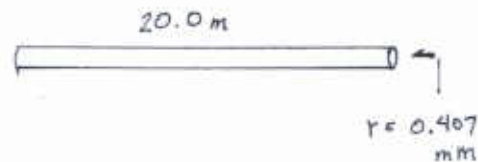2. A copper wire is 20.0 m long; it has a circular cross-section with radius $r = 0.407 \text{ mm}$. [Copper has a resistivity of $1.72 \times 10^{-8} \Omega \cdot \text{m}$.]



What is the resistance of the wire?


Using $A = \pi r^2$, cross-sectional area is

$$A = \pi (0.407 \times 10^{-3} \text{ m})^2 = 5.2 \times 10^{-7} \text{ m}^2$$

Using $R = \rho \frac{L}{A}$, resistance is

$$R = (1.72 \times 10^{-8} \Omega \cdot \text{m}) \frac{(20.0 \text{ m})}{(5.2 \times 10^{-7} \text{ m}^2)} = \boxed{0.66 \Omega}$$

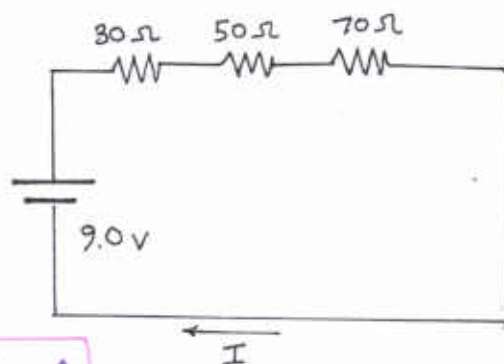3. A circuit consists of a 9.0 V battery connected to a set of resistors, with values 30 Ω , 50 Ω and 70 Ω , as shown in the figure.



a) What is the current in the circuit?

With $R_{eq} = R_{series} = 30\Omega + 50\Omega + 70\Omega = 150\Omega$
then from $V = IR_{eq}$,

$$I = \frac{V}{R_{eq}} = (9.0V) / (150\Omega) = \boxed{6.0 \times 10^{-2} A = 60 mA}$$

b) What is the potential difference (voltage drop) across the 50.0 Ω resistor?

Voltage is given by Ohm's law for that resistor, $V = IR$, so

$$V = (6.0 \times 10^{-2} A)(50\Omega) = \boxed{3.0 V}$$

c) How much energy is dissipated in the 50.0 Ω resistor in one minute?

Use $P = I^2 R$, then power dissipation is

$$P = (6.0 \times 10^{-2} A)^2 (50\Omega) = 0.18 W$$

and in 1 min = 60 s, energy dissipated is

$$E = P \cdot t = (0.18 W)(60 s) = \boxed{10.8 J}$$

You must show all your work and include the right units with your answers!

$$k = \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 \frac{N \cdot m^2}{C^2} \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{C^2}{N \cdot m^2} \quad F = k \frac{|q_1 q_2|}{r^2} = \frac{1}{4\pi\epsilon_0} \frac{|q_1 q_2|}{r^2}$$

$$F = ma \quad g = 9.80 \frac{m}{s^2} \quad m_{elec} = 9.1094 \times 10^{-31} kg \quad e = 1.602 \times 10^{-19} C$$

$$A_{circle} = \pi r^2 \quad \text{Energy} = Pt \quad |E_x| = \left| \frac{\Delta V}{\Delta x} \right| \quad q = CV \quad C = \frac{\epsilon_0 A}{d} \quad \text{Energy} = \frac{1}{2} CV^2$$

$$V = IR \quad R = \rho \frac{L}{A} \quad R_{ser} = R_1 + R_2 + \dots \quad \frac{1}{R_{par}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$P = VI = I^2 R = \frac{V^2}{R}$$