

Phys 2120-4


9/28/12

Note Title


9/28/2012

# Electric Circuits


$$V = IR$$

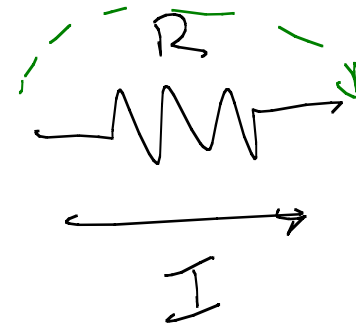

Voltage  
drop  
 $V$

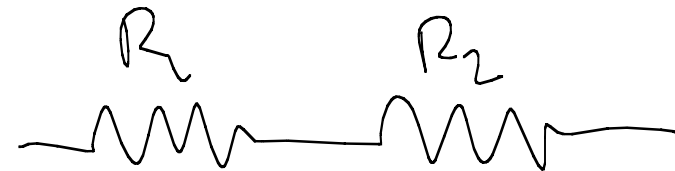

$$R_{eq} = R_1 + R_2$$

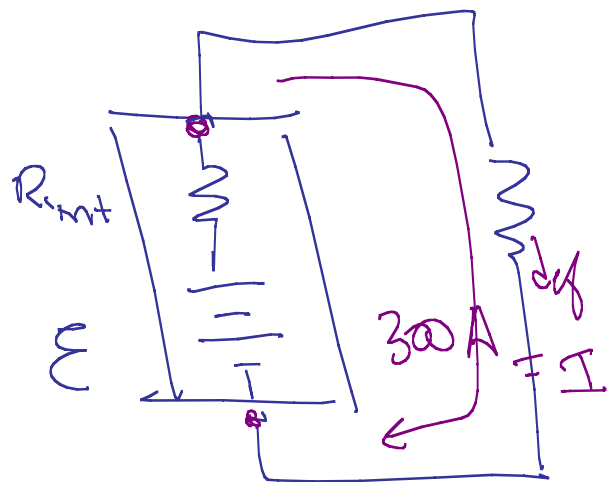

25.21 A defective starting motor draws  $300\text{ A}$  from car's

$12\text{ V}$  battery, dropping the terminal voltage to  $6\text{ V}$ .

A good starter would draw only  $100\text{ A}$ . What is terminal voltage with a good starter?

Terminal voltage is  $6\text{ V}$


$$\mathcal{E} - IR_{int} = 6\text{ V}$$

$$R_{int} = \frac{6\text{ V}}{300\text{ A}} = 0.020\ \Omega \quad \mathcal{E} = 12\text{ V}$$

---

with  $100\text{ A}$   $V_{tw} = 12 - IR_{int} = 10\text{ V}$

## Resistors in Parallel!

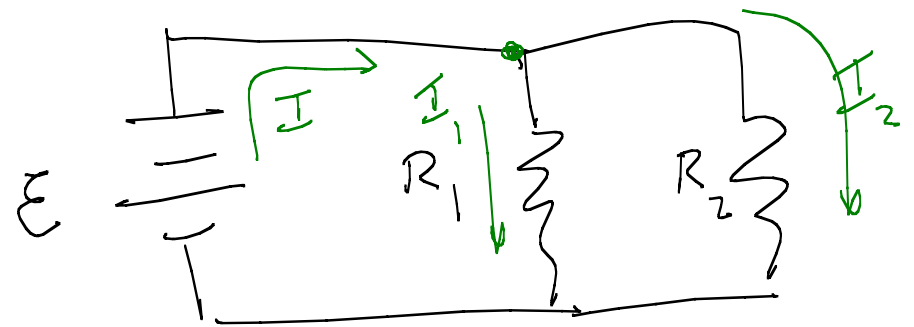

$$I = I_1 + I_2$$

Voltage drop across either is  $\mathcal{E}$

$$\mathcal{E} = I_1 R_1 \quad \mathcal{E} = I_2 R_2$$

$$I_1 = \frac{\mathcal{E}}{R_1} \quad I_2 = \frac{\mathcal{E}}{R_2}$$

$$I = \frac{\mathcal{E}}{R_1} + \frac{\mathcal{E}}{R_2} = \mathcal{E} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \mathcal{E} \left( \frac{R_1 + R_2}{R_1 R_2} \right)$$


$$\mathcal{E} = I \left( \frac{R_1 R_2}{R_1 + R_2} \right) = I R_{eq}$$

$$\left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$R_{eq} = \left( \frac{R_1 R_2}{R_1 + R_2} \right) = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Add reciprocals

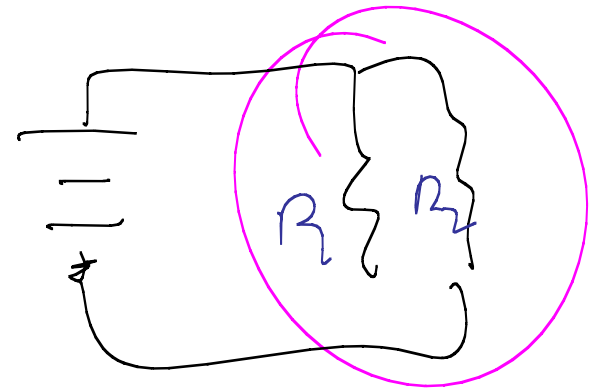


In general,



$$\frac{1}{R_{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \right)$$

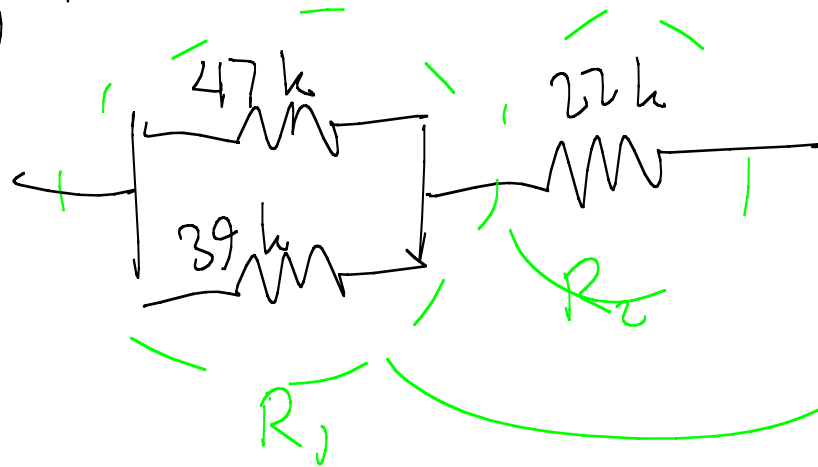25.19

A  $47\text{ k}\Omega$  and a  $39\text{ k}\Omega$  resistor are in parallel and the pair is in series with a  $22\text{ k}\Omega$  resistor. What's the resistance of the combination?




$$\frac{1}{R_1} = \frac{1}{47\text{ k}\Omega} + \frac{1}{39\text{ k}\Omega}$$

$$R_1 = 21.3\text{ k}\Omega$$

$$R_1 + R_2 = 21.3\text{ k}\Omega + 22\text{ k}\Omega = 43.3\text{ k}\Omega$$

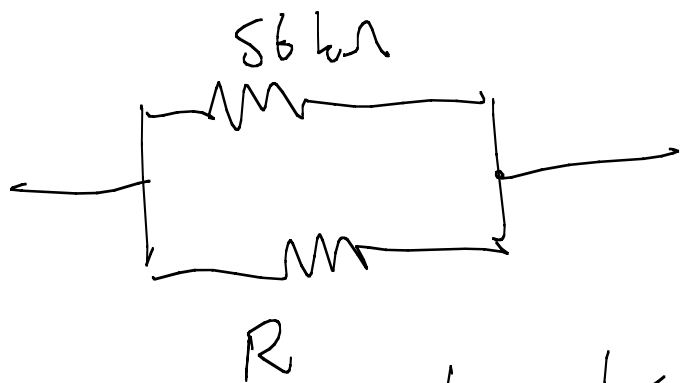25.20 What resistance should you place in parallel with a  $56\text{ k}\Omega$  resistor to make an equivalent res. of  $45\text{ k}\Omega$ ?




$$= 45\text{ k}\Omega = R_{eq}$$

$$R = 230\text{ k}\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{45\text{ k}\Omega} = \left( \frac{1}{56\text{ k}\Omega} + \frac{1}{R} \right)$$

2536

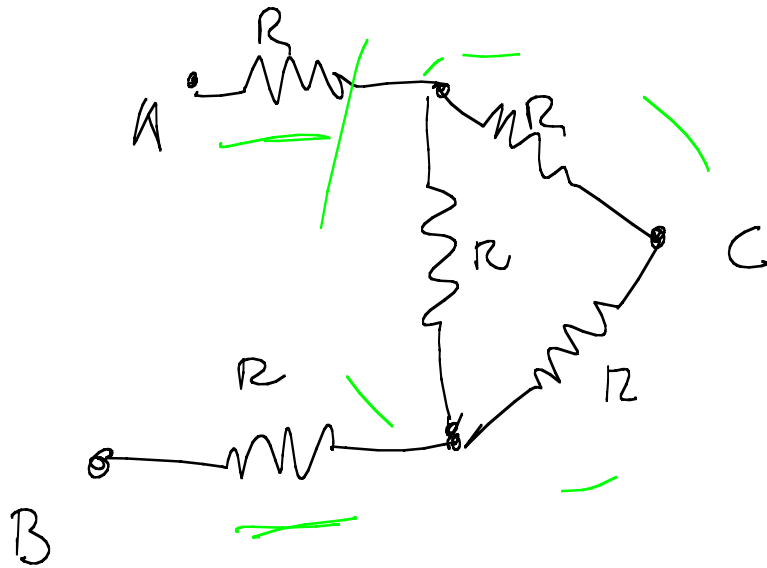

All resistors have same value  $R$

Find resistance

a) Between A and B

b) Between A and C

a) Series of 3 things  
In middle





$$\frac{1}{R_{eq}} = \frac{1}{R} + \frac{1}{2R} = \frac{3}{2R}$$

$$R_{eq} = \frac{2}{3}R = 0.667R$$

$$R_{\text{Tot}} = R + 0.667R + R = 2.667R$$

A to C

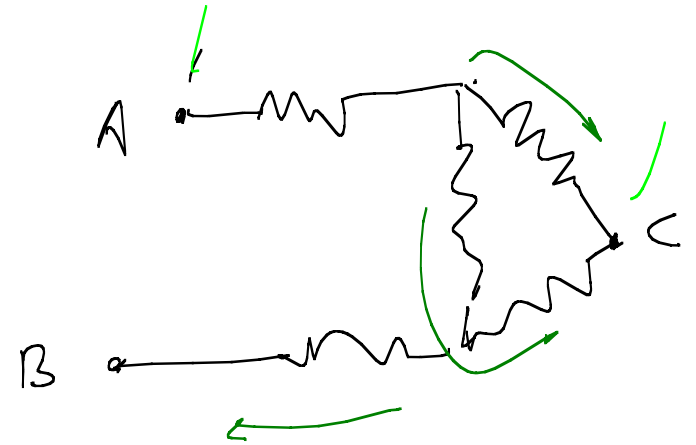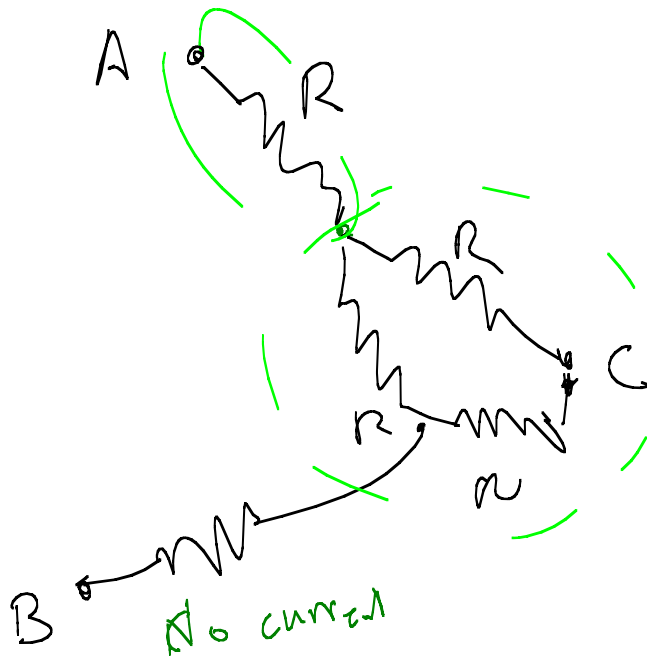

$$R_{eq} = R + 0.667R = 1.667R$$



25.37 In last problem take  $R$  to be  $1\text{ k}\Omega$ .


Find current in vertical resistor when a  $6.0\text{ V}$  battery is connected between A & B

In prev. prob.

$$R_{\text{Total}} = 2.667\text{ k}\Omega$$

$$I = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{6.0\text{ V}}{2.667\text{ k}\Omega} =$$

$$2.25 \times 10^{-3}\text{ A}$$

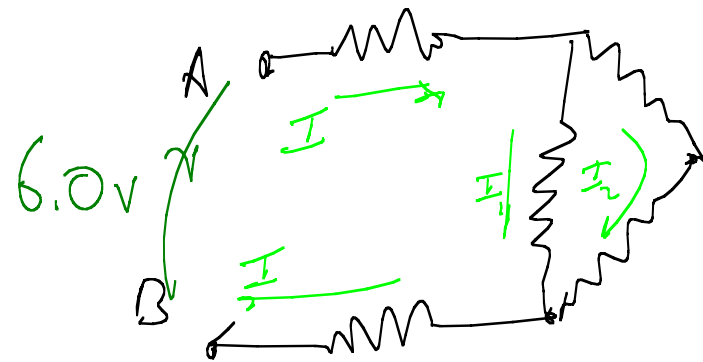

With  $I$  find drops across first & last resistor

Each is  $V = (2.25 \times 10^{-3} \text{ A})(1 \text{ k}\Omega) = 2.25 \text{ V}$

So 
$$V_{\text{vert}} = 6.0 \text{ V} - 2.25 \text{ V} - 2.25 \text{ V}$$
$$= 1.50 \text{ V}$$

Current in vertical resist. is

$$I = \frac{1.50 \text{ V}}{1 \text{ k}\Omega} = 1.50 \times 10^{-3} \text{ A} = 1.5 \text{ mA}$$

For more complicated circuits, must use  
Kirchhoff's Laws.



Solving for current

1)  $I_1 + I_2 + I_3$

$= I_4$






Current:

What goes in must come out.

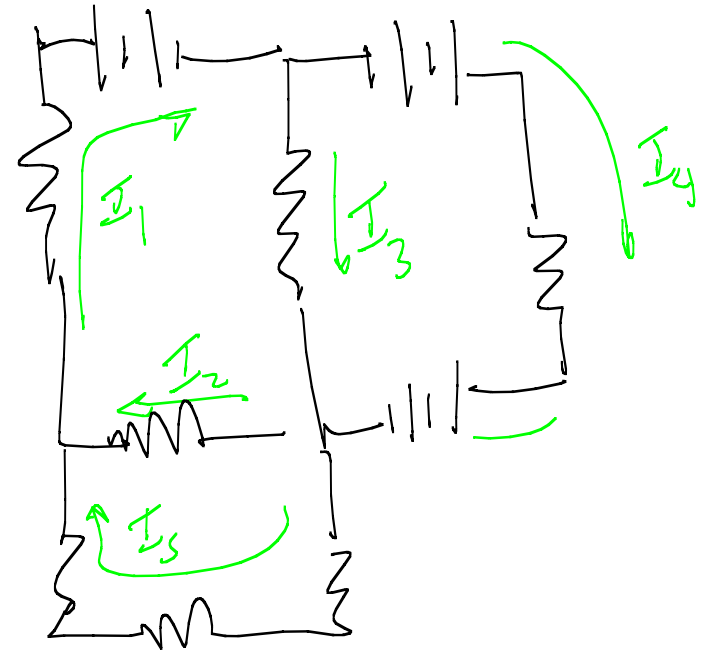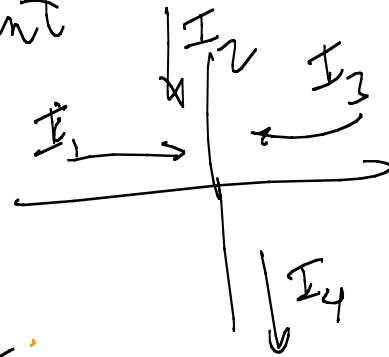

Consider loops in circuit

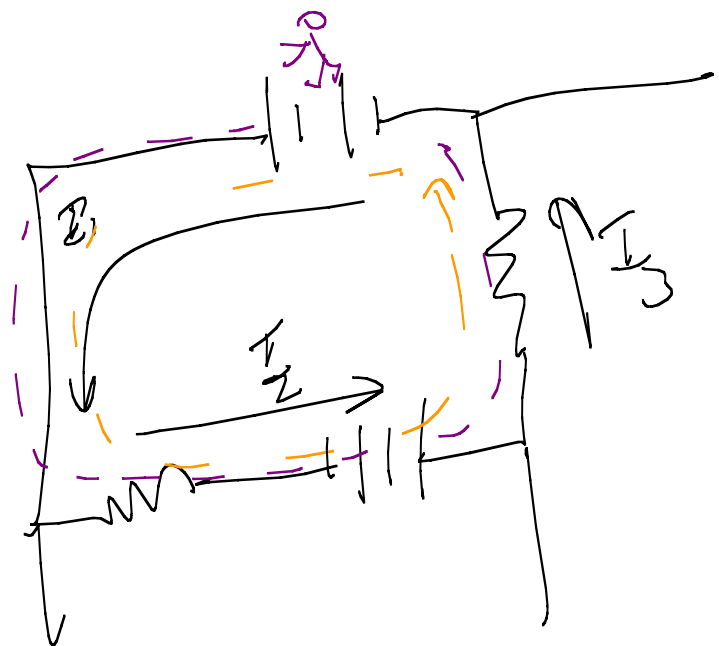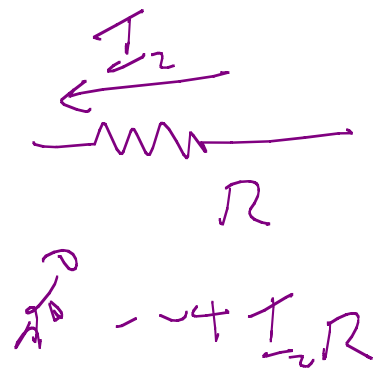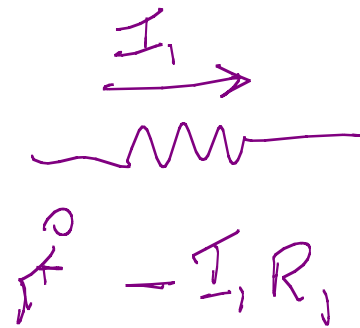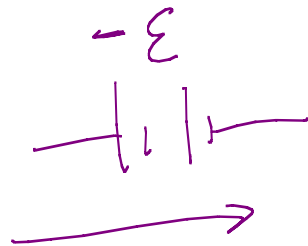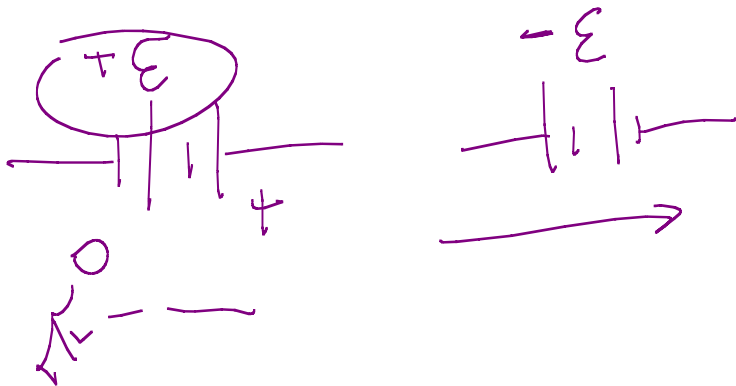2) Voltage gains & drops seen by little man add up to zero.




25.25 Take  $E_2$  25.13 replace:  $E_2 = 1.0 \text{ V}$   
Solve it!

Top junction:

$$I_1 = I_2 + I_3$$

Loop 1 Little man sees

$$+6 \text{ V} - I_1 (2\Omega) - I_3 (1\Omega) = 0$$

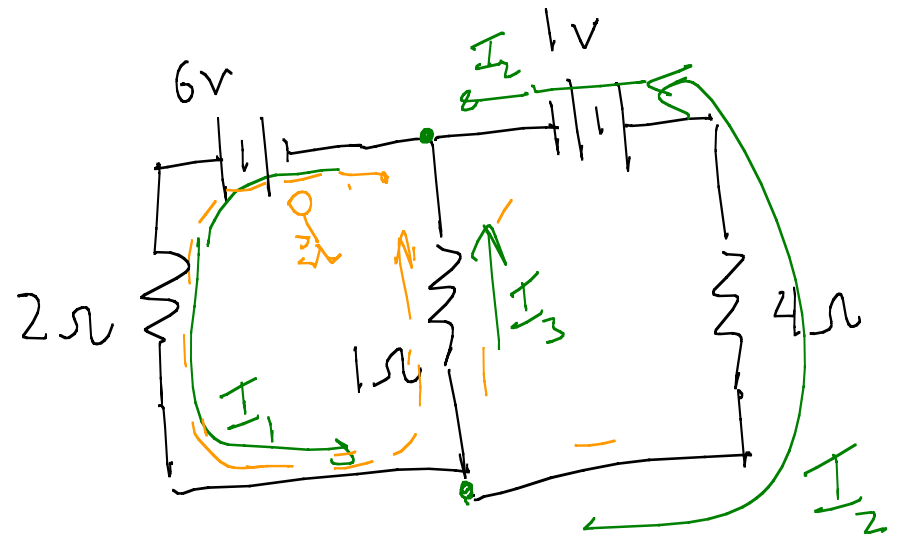

loop 2:

$$1V + 4\Omega I_2 - I_3(1\Omega) = 0$$