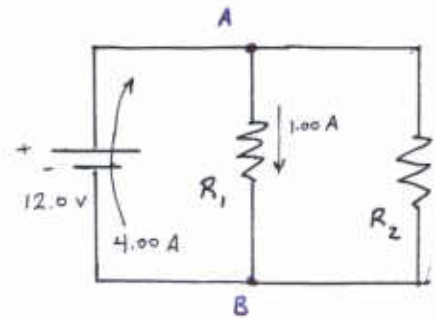


Name _____

Phys 122 — Section 1

Quiz #2

1. In the simple circuit shown here, resistors R_1 and R_2 are connected in parallel across a battery of voltage 12.0 V. The *total* current (i.e. through the battery) is 4.00 A. The current through R_1 is 1.00 A.



a) What is potential drop across R_1 ?

Same as the battery voltage: 12.0 V

b) What is potential drop across R_2 ?

" : 12.0 V

$$V_{AB} = 12.0 \text{ V}$$

c) What is the current I_2 through R_2 ?

At junction A 4.00 A goes in and 1.00 A goes out along one branch. So 3.00 A must go out along the other branch

d) What is the value of R_1 ?

Ohm's Law for R_1 gives $R_1 = \frac{V_1}{I_1} = \frac{12.0 \text{ V}}{1.00 \text{ A}} = 12.0 \Omega$

e) What is the value of R_2 ?


Ohm's Law for R_2 gives $R_2 = \frac{V_2}{I_2} = \frac{12.0 \text{ V}}{3.00 \text{ A}} = 4.0 \Omega$

2. A $2.00 \text{ k}\Omega$ and a $3.00 \text{ k}\Omega$ resistor are connected in series across a 10.0 V battery.

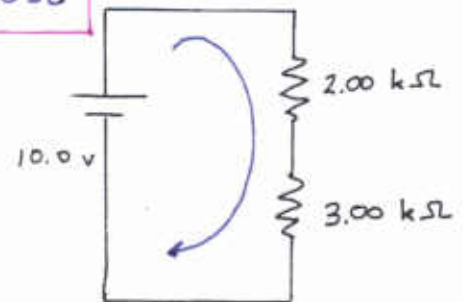a) Find the current in this circuit.

The equivalent resistance is $R_{eq} = 2.00 \text{ k}\Omega + 3.00 \text{ k}\Omega = 5.00 \times 10^3 \Omega$
So the (total) current is

$$I = \frac{V}{R_{eq}} = \frac{10.0 \text{ V}}{5.00 \times 10^3 \Omega} = 2.00 \times 10^{-3} \text{ A} = 2.00 \text{ mA}$$



(Same current as in either resistor.)

b) How much charge flows past any point in the circuit in 10.0 seconds?

Since the current at any point in the circuit is $2.00 \times 10^{-3} \text{ A}$, the charge which passes in 10.0 s is

$$q = It = (2.00 \times 10^{-3} \text{ A})(10.0 \text{ s}) = 2.00 \times 10^{-2} \text{ C}$$

c) What is the power dissipated in the $2.00 \text{ k}\Omega$ resistor?

Power dissipated in this resistor is


$$P = I^2 R = (2.00 \times 10^{-3} \text{ A})^2 (2.00 \times 10^3 \Omega) = 8.00 \times 10^{-3} \text{ W}$$

3. Find the equivalent resistance (from point A to point B) for the combination of resistors shown at the right.

Two parallel 100Ω resistors are equivalent to

$$\frac{1}{R_{\text{par}}} = \frac{1}{100 \Omega} + \frac{1}{100 \Omega} \Rightarrow R_{\text{eq}} = 50 \Omega$$


Giving:

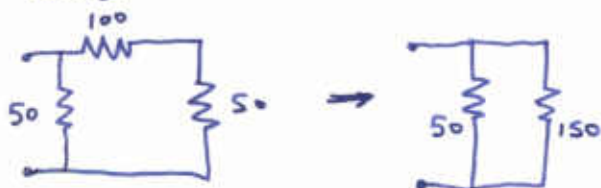

which finally reduces to

$$\frac{1}{R_{\text{eq}}} = \frac{1}{50 \Omega} + \frac{1}{150 \Omega}$$

$$R_{\text{eq}} = 37.5 \Omega$$

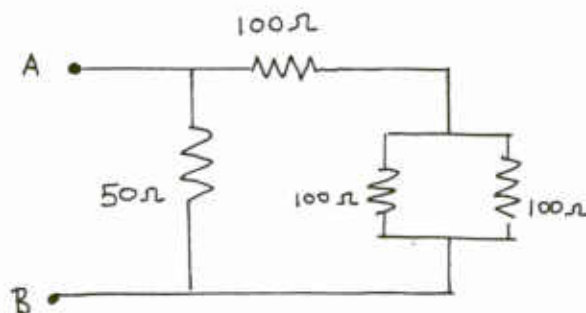

You must show all your work!

$$I = \frac{q}{t} \quad V = IR \quad R = \rho \frac{\ell}{A} \quad P = VI = I^2 R = \frac{V^2}{R} \quad q = CV \quad \text{Energy} = Pt$$

$$R_{\text{ser}} = R_1 + R_2 + \dots \quad \frac{1}{R_{\text{par}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \quad \frac{1}{C_{\text{par}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \quad C_{\text{par}} = C_1 + C_2 + \dots$$

$$\text{Circle: } C = 2\pi R \quad A = \pi R^2 \quad \text{Sphere: } A = 4\pi R^2 \quad V = \frac{4}{3}\pi R^3$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} \quad I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

Some EM units: Coulomb, Volt, Farad, Ampere, Watt, Ohm

Sum of currents going into junction equals sum of currents coming out of junction; around any closed loop, the sum of potential gains equals the sum of potential drops.