

Phys 2120-4

10/29/12


Note Title

10/29/2012

Recap:





R

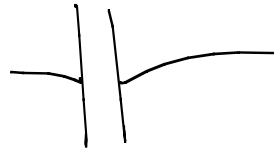

C




L

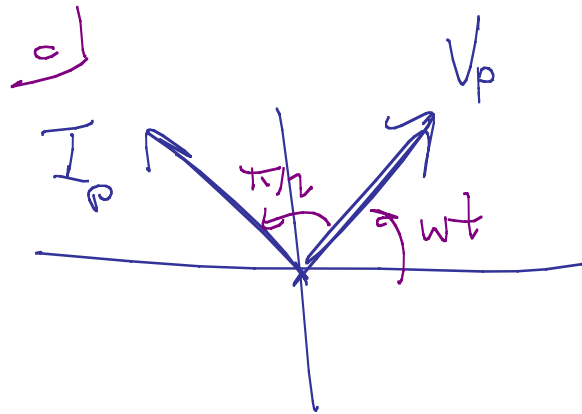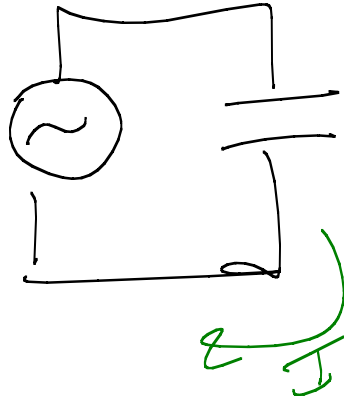


$$I_p = \frac{V_p}{1/\omega C}$$


$$X_C = \frac{1}{\omega C}$$

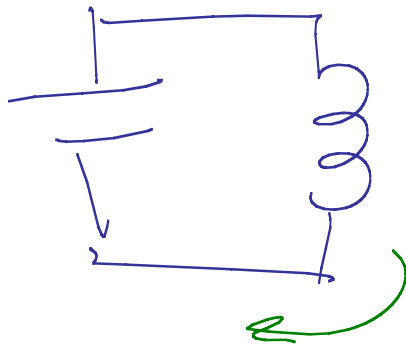

$$\omega = \frac{1}{\sqrt{LC}}$$


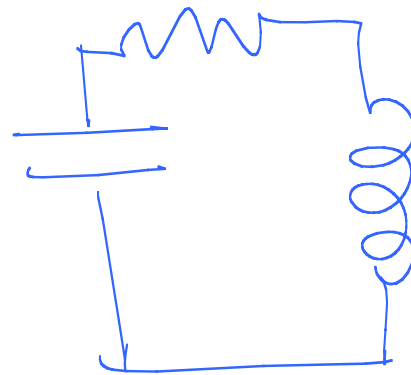


Damped
oscillation.

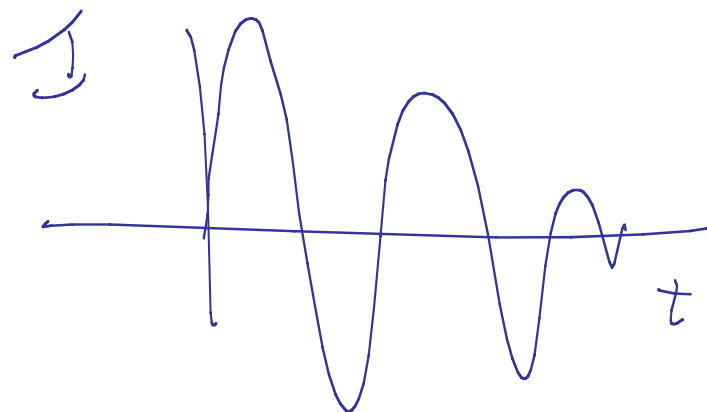

Driven RLC

Mechanical analogy

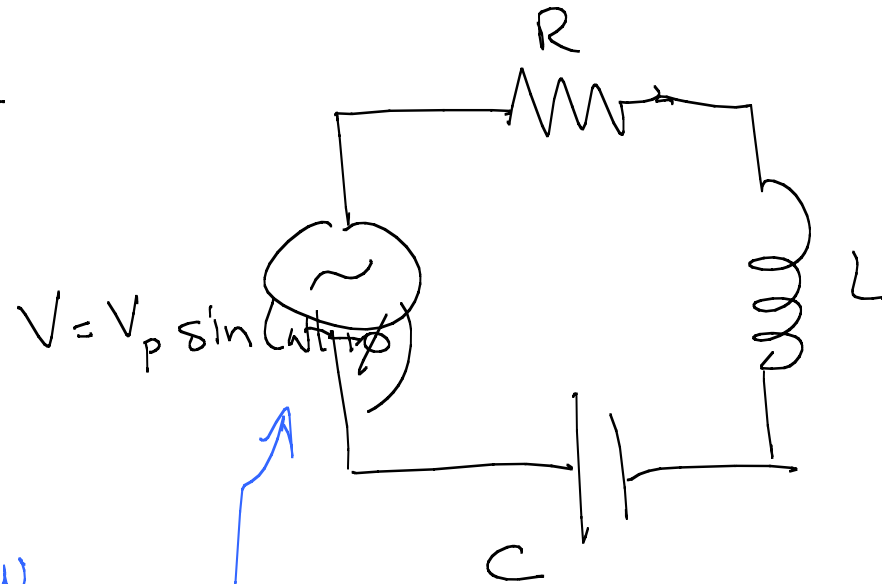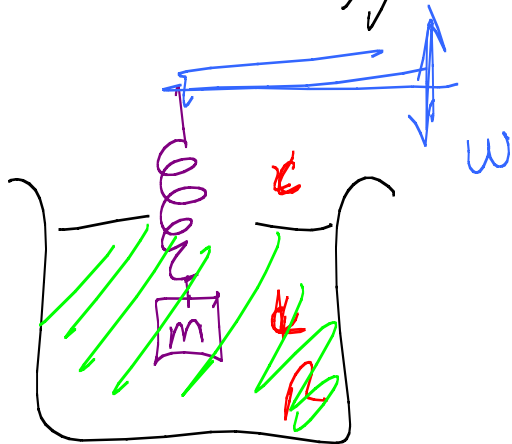

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Phasor $\rightarrow I_p(t)$, \checkmark