

Phys 2120, Section 3
Quiz #3 — Spring 2003


1. a) For the circuit of capacitors shown at the right, find the equivalent capacitance.

Two $6.0\ \mu\text{F}$ cap's in series become:

$$\frac{1}{R_g} = \frac{1}{6.0\ \mu\text{F}} + \frac{1}{6.0\ \mu\text{F}} = 0.333\ \mu\text{F}^{-1} \quad R_g = 3.0\ \mu\text{F}$$

With this (equiv) capacitor in parallel with the $5.0\ \mu\text{F}$ and $4.0\ \mu\text{F}$, get:
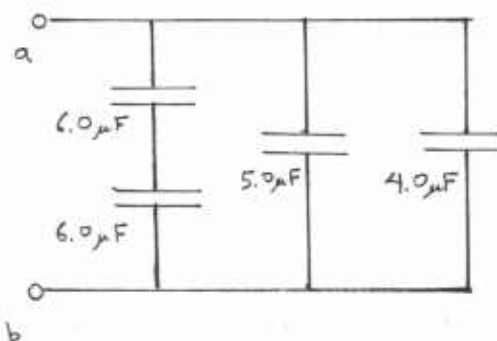
$$R_{eq} = 3.0\ \mu\text{F} + 5.0\ \mu\text{F} + 4.0\ \mu\text{F} = \boxed{12.0\ \mu\text{F}}$$



- b) When a potential difference of $9.00\ \text{V}$ is applied across the leads ab , find the charge on the $5.00\ \mu\text{F}$ capacitor.

Then the pot'l diff. across the $5.0\ \mu\text{F}$ cap is also $9.0\ \text{V}$ so the charge stored is

$$q = CV = (5.0 \times 10^{-6}\ \text{F})(9.0\ \text{V}) = \boxed{4.5 \times 10^{-5}\ \text{C}}$$

- c) Again, with $V_{ab} = 9.0\ \text{V}$, find the charge on either one of the $6.00\ \mu\text{F}$ capacitors.

As found in (a), the series comb of the $6.0\ \mu\text{F}$ cap's has an equiv. cap. of $3.0\ \mu\text{F}$. With $9.0\ \text{V}$ across the pair, the charge stored is

$$q = C_{eq} V = (3.0 \times 10^{-6}\ \text{F})(9.0\ \text{V}) = 2.7 \times 10^{-5}\ \text{C}$$

This is equal to the charge stored on any one of the series capacitors. So the charge on either $6.00\ \mu\text{F}$ cap. is

$$\boxed{2.7 \times 10^{-5}\ \text{C}}$$

2. A certain type of copper wire has a circular cross-section of diameter 1.30 mm.

What length of this wire has a resistance of 0.500Ω ?

With x-sec area $A = \pi r^2 = \pi d^2/4$, use $R = \rho \frac{L}{A}$ and solve for L :

$$L = \frac{RA}{\rho} = \frac{(0.500 \Omega) \pi (1.30 \times 10^{-3} \text{ m})^2 / 4}{(1.69 \times 10^{-8} \Omega \cdot \text{m})} = \boxed{39.3 \text{ m}}$$

3. a) For the circuit shown, find the total current i .


Equiv. resistance of set of three resistors:

$$R_1 \& R_2: \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4.00 \text{ k}\Omega} + \frac{1}{6.00 \text{ k}\Omega}$$

$$R_{eq} = 2.4 \text{ k}\Omega$$

$$R_{eq} \& R_3: R'_{eq} = 2.4 \text{ k}\Omega + 3.00 \text{ k}\Omega = 5.4 \text{ k}\Omega$$
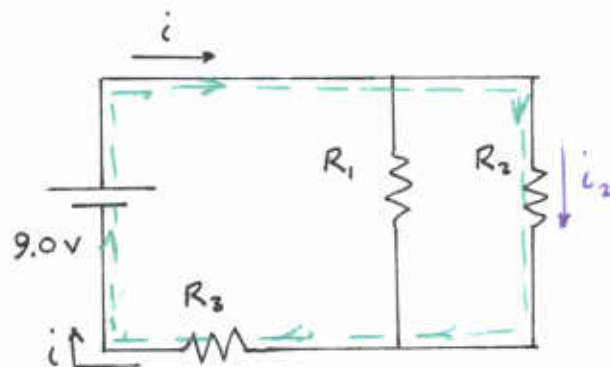
$$i = \frac{V}{R'_{eq}} = \frac{(9.00 \text{ V})}{(5.4 \text{ k}\Omega)} = \boxed{1.67 \times 10^{-3} \text{ A}}$$



$$R_1 = 4.00 \text{ k}\Omega$$

$$R_2 = 6.00 \text{ k}\Omega$$

$$R_3 = 3.00 \text{ k}\Omega$$

b) Find the current in R_2 . (The Kirchhoff loop rule may be of help.)

Using the big loop shown (with i_2 as the current thru R_2)

get:

$$+9.0 \text{ V} - i_2 R_2 - i R_3 = 0$$

Solve for i_2 :

$$i_2 R_2 = 9.0 \text{ V} - i R_3 = 9.0 \text{ V} - (1.67 \times 10^{-3} \text{ A})(3.00 \times 10^3 \Omega) = 4.00 \text{ V}$$

$$i_2 = \frac{4.00 \text{ V}}{6.00 \times 10^3 \Omega} = \boxed{6.67 \times 10^{-4} \text{ A}}$$

You must show all your work and include the right units with your answers!

$$q = CV \quad C = \epsilon_0 \frac{A}{d} \quad C = \kappa C_{\text{air}} \quad C_{\text{par}} = C_1 + C_2 + \dots \quad \frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

$$i = \frac{dq}{dt} \quad J = i/A \quad V = iR \quad R = \rho \frac{L}{A} \quad R_{\text{series}} = R_1 + R_2 + \dots \quad \frac{1}{R_{\text{par}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\rho_{\text{Cu}} = 1.69 \times 10^{-8} \Omega \cdot \text{m} \quad \alpha_{\text{Cu}} = 4.3 \times 10^{-3} \text{ K}^{-1}$$

$$\tau = RC \quad q(t) = C\mathcal{E}e^{-t/\tau} \quad i(t) = \frac{\mathcal{E}}{R}e^{-t/\tau}$$