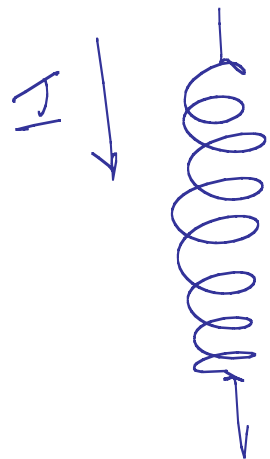


Self-inductance



Inductor,

L

solenoid

$$L = \mu_0 n^2 A l$$

$$\mathcal{E} = -L \frac{dI}{dt}$$




$$\frac{d\Phi_B}{dt} \Rightarrow \mathcal{E} \propto \frac{dI}{dt}$$




opposes it

$$n = \frac{N}{l} \quad \underline{\text{Henry}}$$


RL circuit

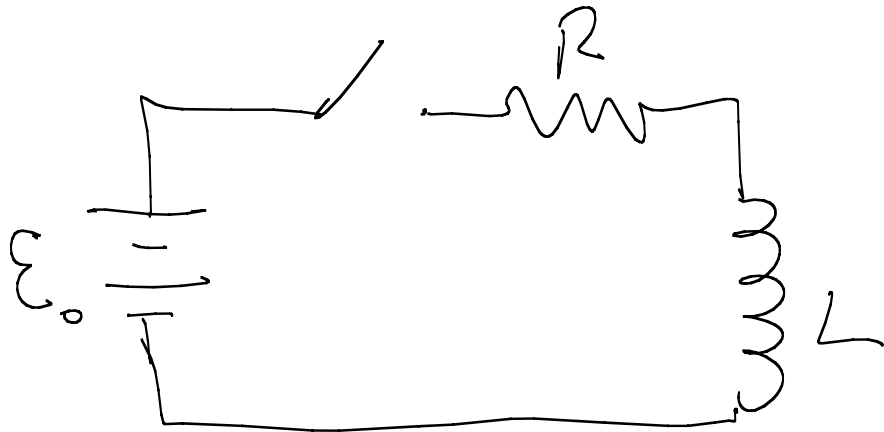

Expect

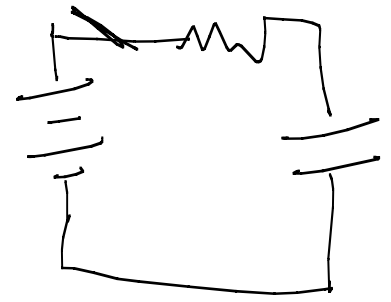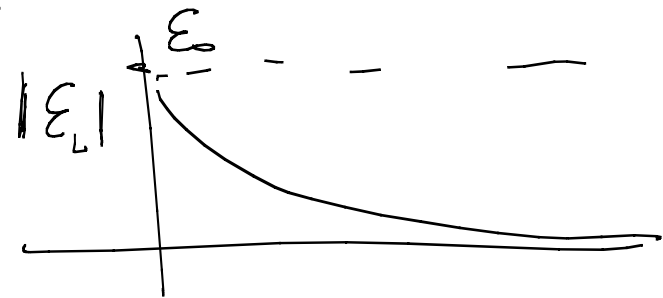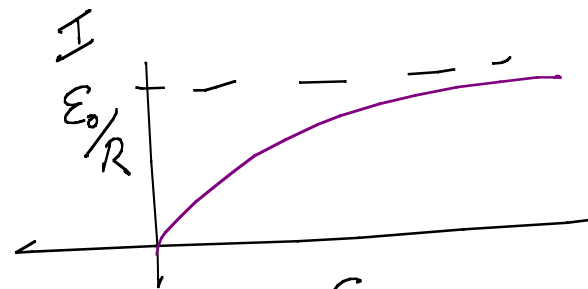

RC

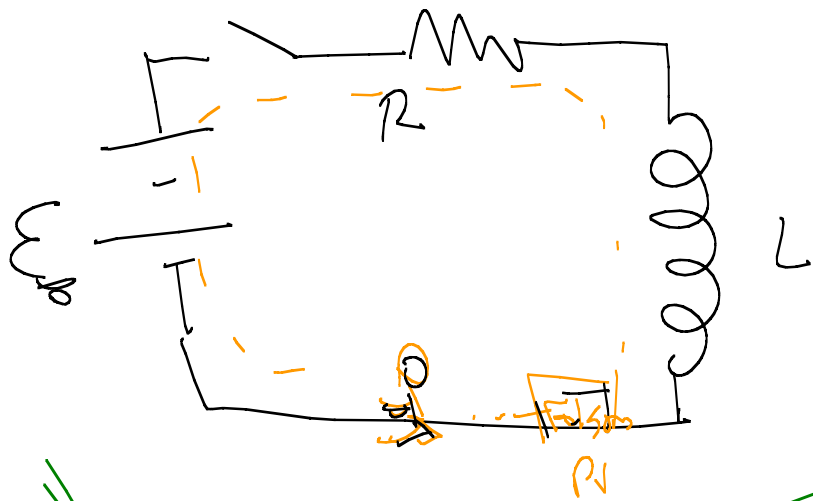

$$E_0 - IR - L \frac{dI}{dt} = 0 \quad (1)$$

Use $\mathcal{E}_L = -L \frac{dI}{dt}$

Substitute in (1), take d/dt (1)

Eqn gives

$$R/L \mathcal{E}_L + d\mathcal{E}_L/dt = 0$$

V_L

$$\frac{dI}{dt} = -\frac{1}{L} \mathcal{E}_L$$



$$\frac{d\mathcal{E}}{dt} = -R/L \mathcal{E}_L \quad \mathcal{E}_L \propto e^{-Rt/L}$$


$$\mathcal{E}_L = (-\mathcal{E}_0) e^{-t/[L/R]}$$

Time constant $\tau_L = L/R$


Current $-L \frac{dI}{dt} = -\mathcal{E}_0 e^{-t/\tau}$

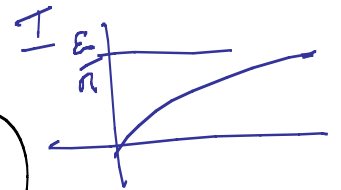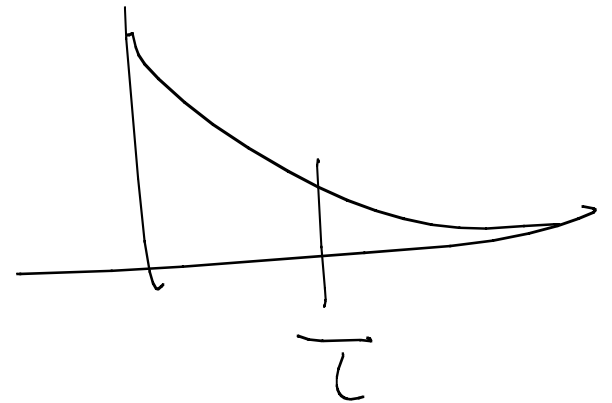Substitute (1) $IR = \mathcal{E}_0 (1 - e^{-t/\tau})$



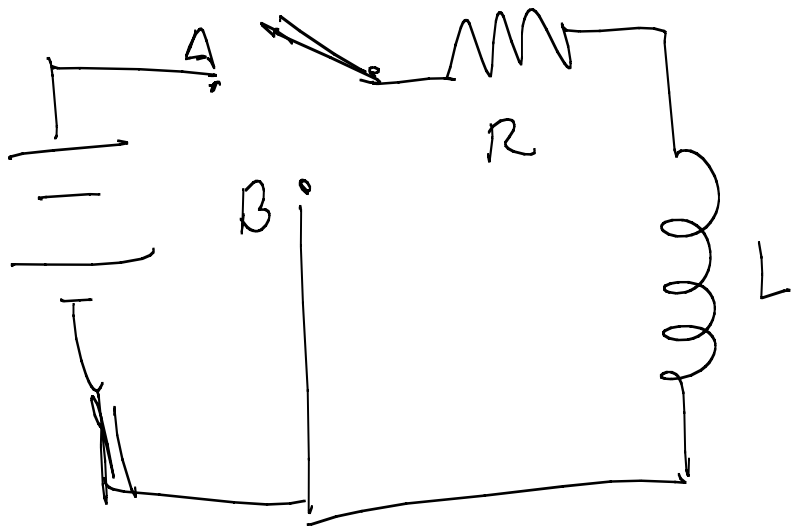

→ A current is constant.

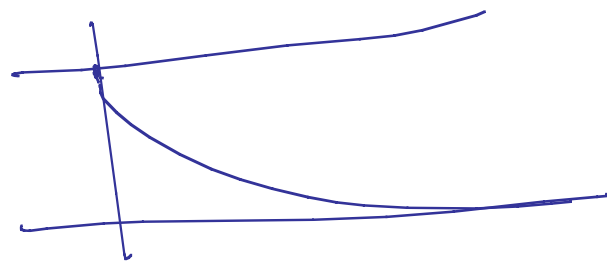

$$Q = CV$$

$$U = \frac{1}{2} CV^2$$

Capacitors store energy

J. Cash's (1) mult by:

E supplied
by battery

$$\mathcal{E} - I^2 R - L I \frac{dI}{dt} = 0$$

Loss $\uparrow E$
in resistor

E "lost" to the inductor.

$$I \mathcal{E}_0 = I^2 R + \frac{d}{dt} \left(\frac{1}{2} L I^2 \right)$$

↑
 \mathcal{E} battery

↑
 \mathcal{E} lost
to res

↑
Rate at which
energy goes
into inductor


$$I \frac{dI}{dt}$$

$$= \frac{L}{2} \frac{d}{dt} (I^2)$$

$$U = \frac{1}{2} L I^2$$

Energy stored in inductor

$$U = \frac{1}{2} C V^2$$

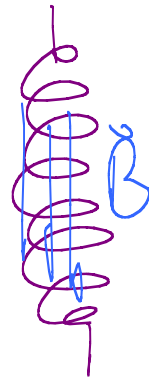

Solenoid: $U = \frac{1}{2} L I^2 = \frac{1}{2} \mu_0 n^2 A l I^2$

Use $B = \mu_0 n I$. Substitute


$$U = \frac{1}{2} \frac{1}{\mu_0} B^2 \underbrace{A l}_{\text{Volume}} = \frac{B^2}{2\mu_0} (\text{Volume})$$




Energy density:

$$u_B = \frac{B^2}{2\mu_0}$$


$$u_E = \frac{1}{2} \epsilon_0 E^2$$

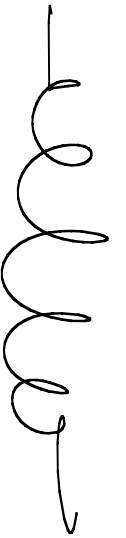

Induced \vec{E} fields

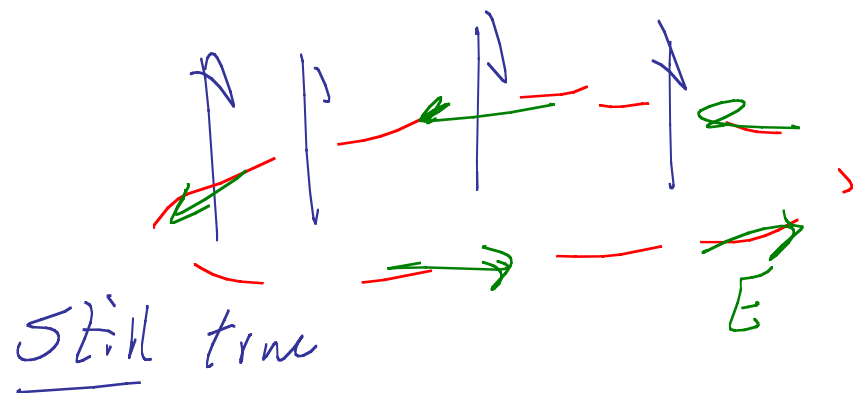
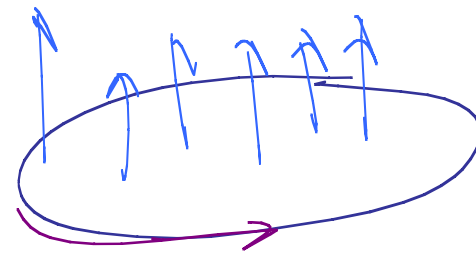
$$\begin{aligned}\mathcal{E} &= \oint \vec{E} \cdot d\vec{r} = - \frac{d\Phi_B}{dt} \\ &= - \frac{d}{dt} \int \vec{B} \cdot d\vec{A}\end{aligned}$$



$$\mathcal{E} = - \frac{d\Phi_B}{dt}$$

$$= - \frac{d}{dt} \int \vec{B} \cdot d\vec{A}$$

even
without wire.

Maxwell Eqns

4 of them


$$\oint \vec{E} \cdot d\vec{A} = \frac{q_{enc}}{\epsilon_0} = \frac{1}{\epsilon_0} \int \rho \, dV$$

$$\oint \vec{E} \cdot d\vec{l} = - \frac{d}{dt} \int \vec{B} \cdot d\vec{A}$$

$$\oint \vec{B} \cdot d\vec{A} = 0$$

$$\oint \vec{B} \cdot d\vec{l} = \mu_0 I_{enc} = \mu_0 \int \vec{J} \cdot d\vec{A}$$



Amperes law note
quite right.

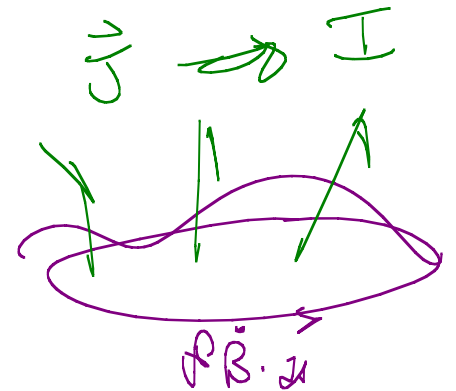

Electrostatics: $\oint \vec{E} \cdot d\vec{r} = 0$


With currents $\oint \vec{E} \cdot d\vec{r} = -\frac{1}{\mu_0} \int \vec{B} \cdot d\vec{l}$

Diamagnetism

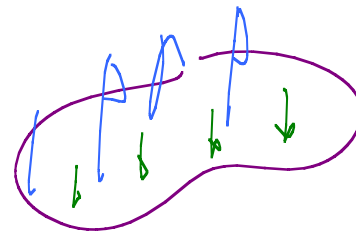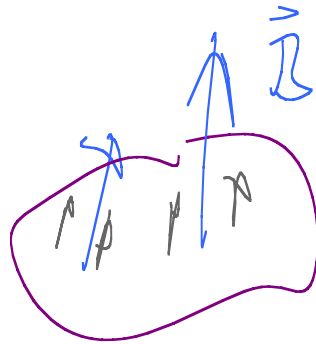

Diamagnetic

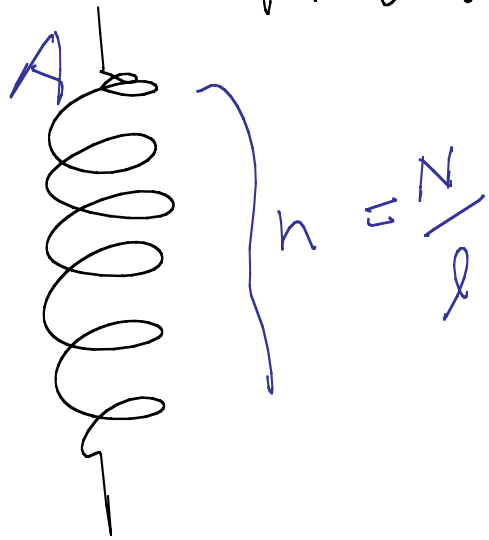27. 17 Find self-inductance of a 1000 turn solenoid 50 cm long, and 4.0 cm in diameter.



$$L = \mu_0 n^2 A l$$

$$\begin{aligned} &= (4\pi \times 10^{-7}) \left(\frac{1000}{0.50} \right)^2 \left(\pi (2.0 \times 10^{-2})^2 \right) \\ &\quad \cdot (0.50) \\ &= 3.2 \text{ mH} \end{aligned}$$

$$= 3.2 \times 10^{-3} \text{ Henry}$$

27.18 The current in an inductor is
charging at 100 A/s & inductor emf
is 40 V . What's self-inductance



$$\mathcal{E} = L \frac{dI}{dt}$$

(ob3 values)

$$L = \frac{\mathcal{E}}{\left(\frac{dI}{dt}\right)} = \frac{40 \text{ V}}{100 \text{ A/s}} = 0.40 \text{ H}$$



27.52 The current in a series RL circuit rises to half its final value in 7.6 s

What's the time constant?

$$I = \frac{\mathcal{E}_0}{R} (1 - e^{-t/\tau})$$

At $t = 7.6 \text{ s}$, $\frac{\mathcal{E}_0}{R} = \frac{I_{\text{final}}}{R}$
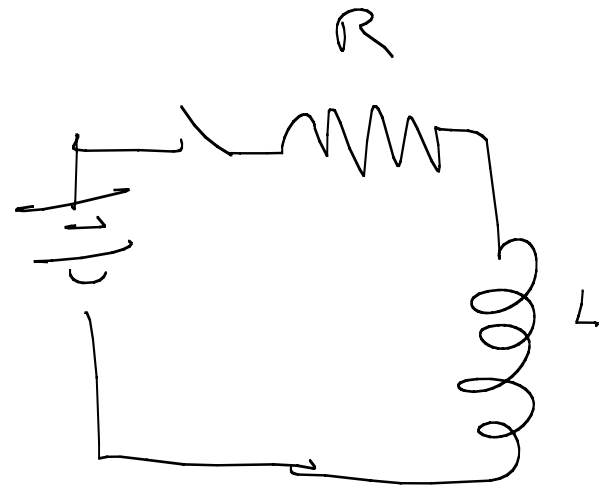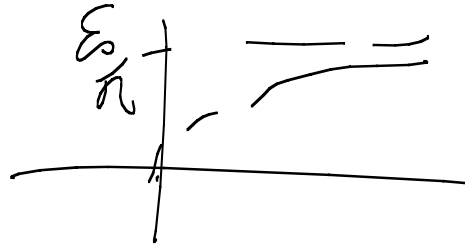
$$(1 - e^{-t/\tau}) = \frac{1}{2} = 0.5$$



Math

$$e^{-t/\tau} = 0.5$$

Find \ln
on
calculator

$$\frac{t}{\tau} = 0.693$$


$$\Rightarrow \tau = 11.05$$

27.53 In series RL circuit $\mathcal{E} = 45\text{V}$
 $R = 3.3\ \Omega$ $L = 2.1\text{ H}$. If current
 is 9.5A how long has switch been closed

$$\frac{\mathcal{E}}{R} = 13.6\text{A}$$

$$9.5\text{A} = 13.6\text{A} (1 - e^{-t/\tau})$$

→ Find t Do math → 0.763s

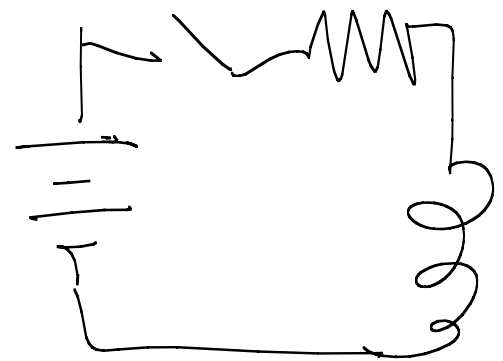

$$\tau = \frac{L}{R} = 0.636\text{s}$$