

## Quiz #3 — Spring 2008

## Phys 2020

1. For the circuit diagrammed at the right,  
a) Find the current in the  $80\ \Omega$  resistor.

In this circuit the  $100\ \Omega$  and  $200\ \Omega$  resistors are in parallel, and *that* combination is in series with the  $80\ \Omega$  resistor.

The equivalent resistance of the  $100 - 200\ \Omega$  combination is

$$\frac{1}{R_{\text{eq}}} = \frac{1}{100\ \Omega} + \frac{1}{200\ \Omega} \quad \Rightarrow \quad R_{\text{eq}} = 66.7\ \Omega$$

The equivalent resistance of the entire circuit is

$$R = 80\ \Omega + 66.7\ \Omega = 146.7\ \Omega$$

and Ohm's law gives the *total* current:

$$I = \frac{V}{R} = \frac{120\ \text{V}}{146.7\ \Omega} = 0.818\ \text{A}$$

and the total current is *the same* as the current in the  $80\ \Omega$  resistor.

- b) Find the current in the  $200\ \Omega$  resistor.

The potential difference across the  $80\ \Omega$  resistor is


$$V_{80} = IR = (0.818\ \text{A})(80\ \Omega) = 65.5\ \text{V}$$

so, adding in this voltage drop, the potential difference across the parallel resistors is


$$V = 120\ \text{V} - 65.5\ \text{V} = 54.5\ \text{V}$$

which is the same as the potential across the  $200\ \Omega$  resistor. Then the *current* in the  $200\ \Omega$  resistor is
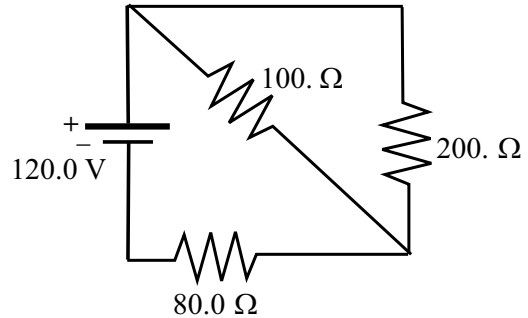
$$I_{200} = \frac{V}{R} = \frac{54.5\ \text{V}}{200\ \Omega} = 0.27\ \text{A}$$



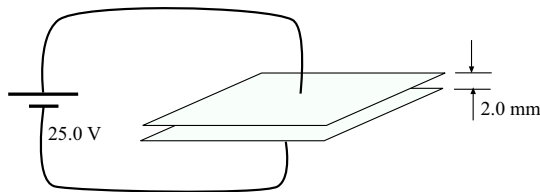2. A capacitor is formed from two flat plates which are separated by a (small) distance of 2.0 mm. A potential difference of 25.0 V is applied to the plates and a charge of 5.00 nC collects on the plates.



a) What is the value of the capacitance?

Use  $Q = CV$ , then


$$C = \frac{Q}{V} = \frac{(5.00 \times 10^{-9} \text{ C})}{(25.0 \text{ V})} = 2.0 \times 10^{-10} \text{ F}$$

b) What is the magnitude of the electric field between the plates (when the voltage is applied)?

Use  $|E_s| = \Delta V / \Delta s$  (this is valid because there is a uniform field between the plates), then

$$E = \frac{(25.0 \text{ V})}{(2.00 \times 10^{-3} \text{ m})} = 1.25 \times 10^4 \frac{\text{V}}{\text{m}}$$

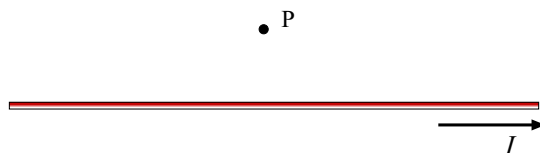3. A long wire carries a current  $I$  as shown at the right; the current is in the plane of the page, as is the point  $P$ .



What is direction of the magnetic field at point  $P$ ? *Briefly* explain how you arrived at your answer.

Using the right-hand rule (thumb in dir of current, fingers wrapping around wire) we find that the magnetic field at  $P$  is out of the page.

**You must show all your work and include the right units with your answers!**

$$e = 1.60 \times 10^{-19} \text{ C} \quad K = 8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2} \quad \epsilon_0 = 8.854 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}$$

$$F = K \frac{|q_1 q_2|}{r^2} \quad \mathbf{F} = q\mathbf{E} \quad E_{\text{pt-ch}} = K \frac{Q}{r^2} \quad E_{\text{par-pl}} = \frac{Q}{\epsilon_0 A}$$

$$\Delta U = Q\Delta V \quad E_s = -\frac{\Delta V}{\Delta s} \quad V_{\text{pt-ch}} = K \frac{Q}{r} \quad Q = C(\Delta V_C) \quad C = \kappa \frac{\epsilon_0 A}{d}$$

$$I = \frac{Q}{\Delta t} \quad V = IR \quad P = VI = I^2 R \quad R_{\text{ser}} = R_1 + R_2 + \dots \quad \frac{1}{R_{\text{par}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$