

Phys 2120-4


10/26/12

Note Title

10/26/2012


AC Circuit

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

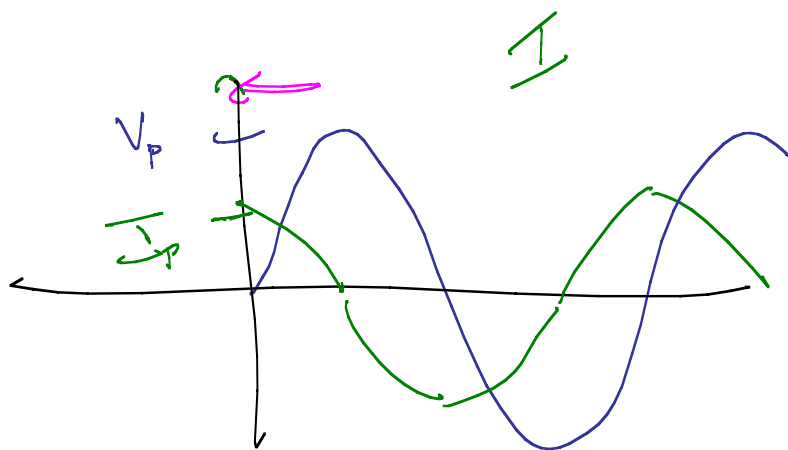

Current leads voltage

$$v(t) = V_p \sin \omega t$$

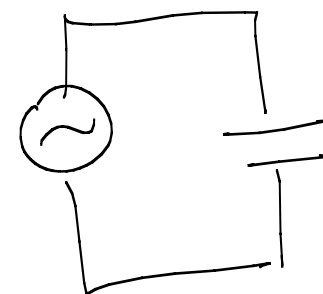


Frequency



$I(t)$

$$I_p = \frac{V_p}{X_c} \quad X_c = \frac{1}{\omega C} \text{ ohms}$$
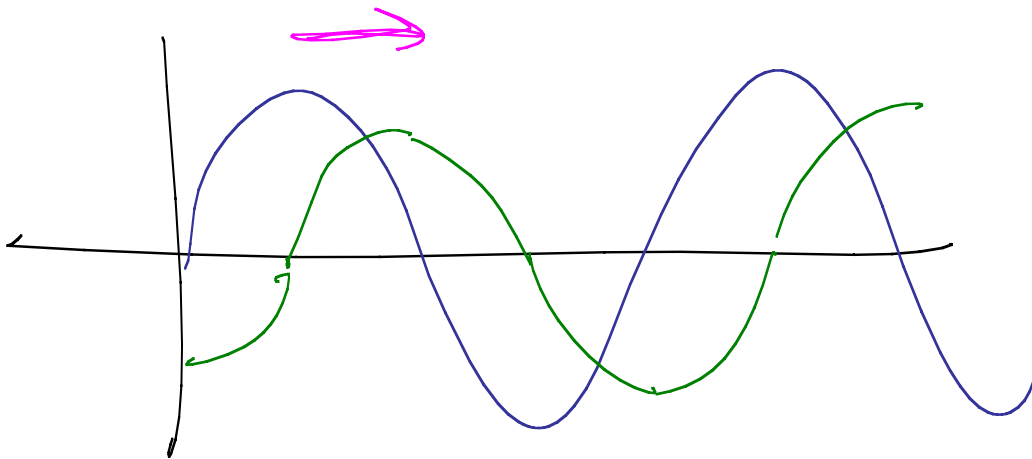
$$I_p = \frac{V_p}{X_L} \quad X_L = \omega L$$



Current lags the voltage

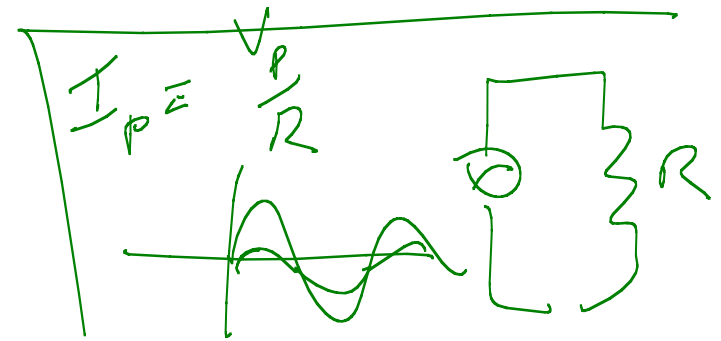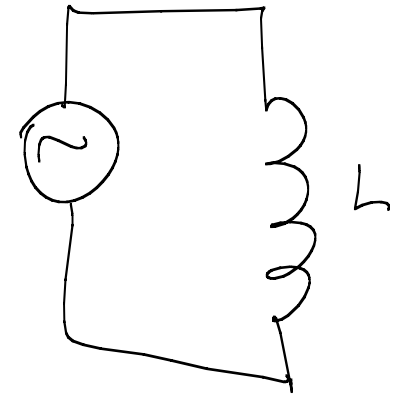

28.13 Find the rms current in a $1.0 \mu\text{F}$ capacitor conn'd across 120-V rms $60 \frac{1}{3}$ AC power


$$\omega = 2\pi f = 377 \text{ s}^{-1}$$

$$X_c = \frac{1}{\omega C} = 2.65 \times 10^3 \Omega_{\text{rms}}$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_c} = \frac{120 \text{ V}}{2.65 \times 10^3 \Omega} = 45 \text{ mA}$$

$$V_p = \sqrt{2} (120 \text{ V})$$

~~~~~

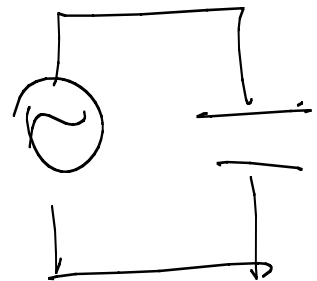





28.19  $470\ \Omega$  Res,  $10\ \mu\text{F}$  capacitor,  $750\text{ mH}$  inductor  
 are each connected across  $6.3\text{ V rms}$   $60\text{ Hz}$   
 $\omega = 2\pi f$   
 AC power. Find the rms current

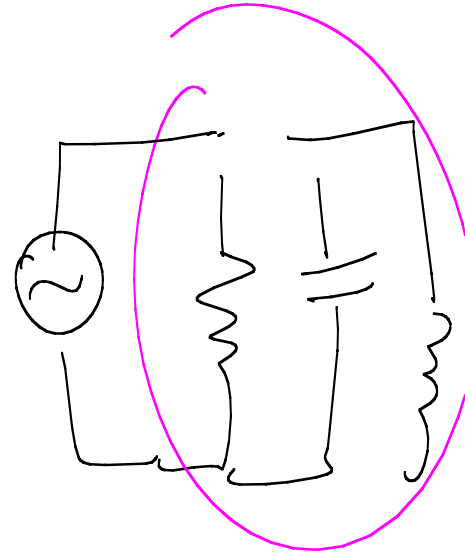a) R:  $I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = 13\text{ mA}$


C:  $I_{\text{rms}} = \frac{V_{\text{rms}}}{\frac{1}{\omega C}} = \omega C V_{\text{rms}} = 24\text{ mA}$

L:  $I_{\text{rms}} = \frac{V_{\text{rms}}}{\frac{1}{\omega L}} = \omega L V_{\text{rms}} = 22\text{ mA}$



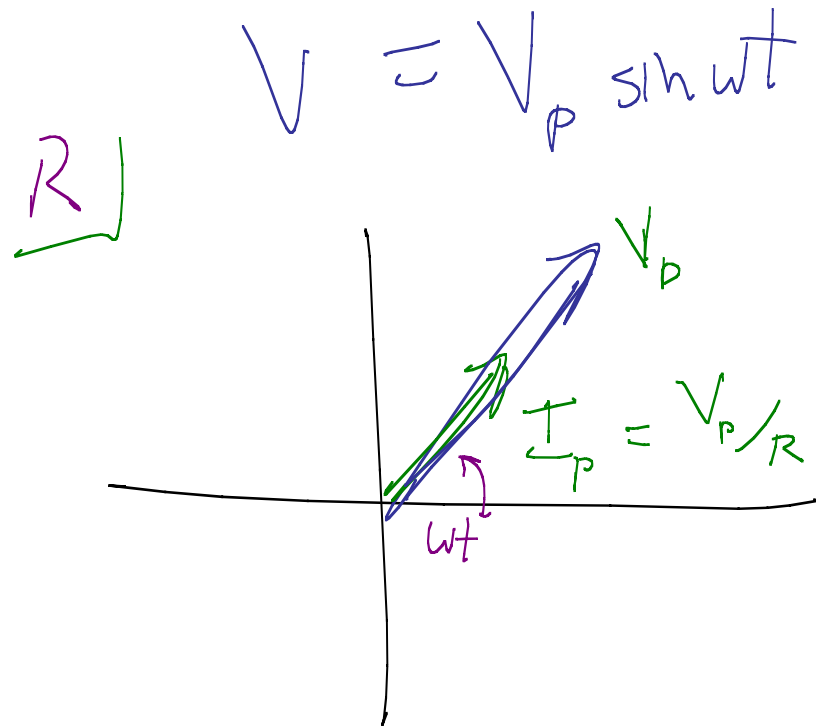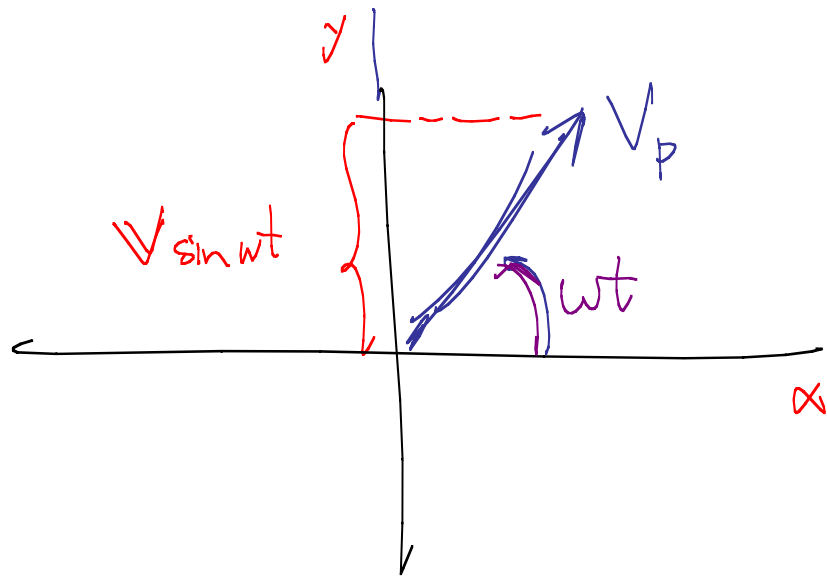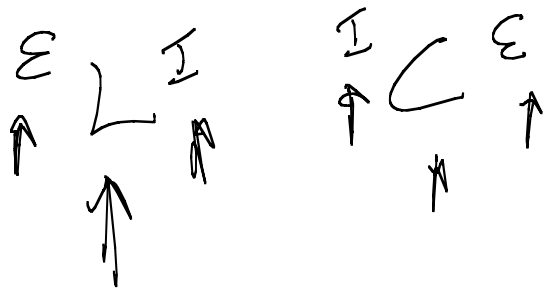


c)

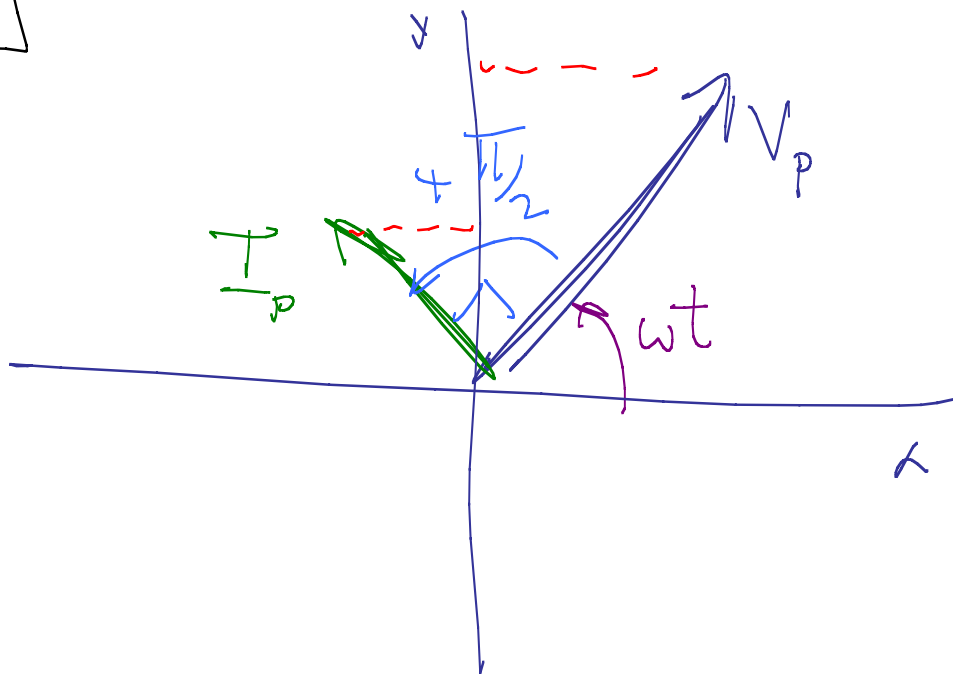

$$I = \underbrace{\omega C V_p}_{I_p} \sin\left(\omega t + \frac{\pi}{2}\right)$$

$$I_p = \frac{V_p}{\frac{1}{\omega C}}$$

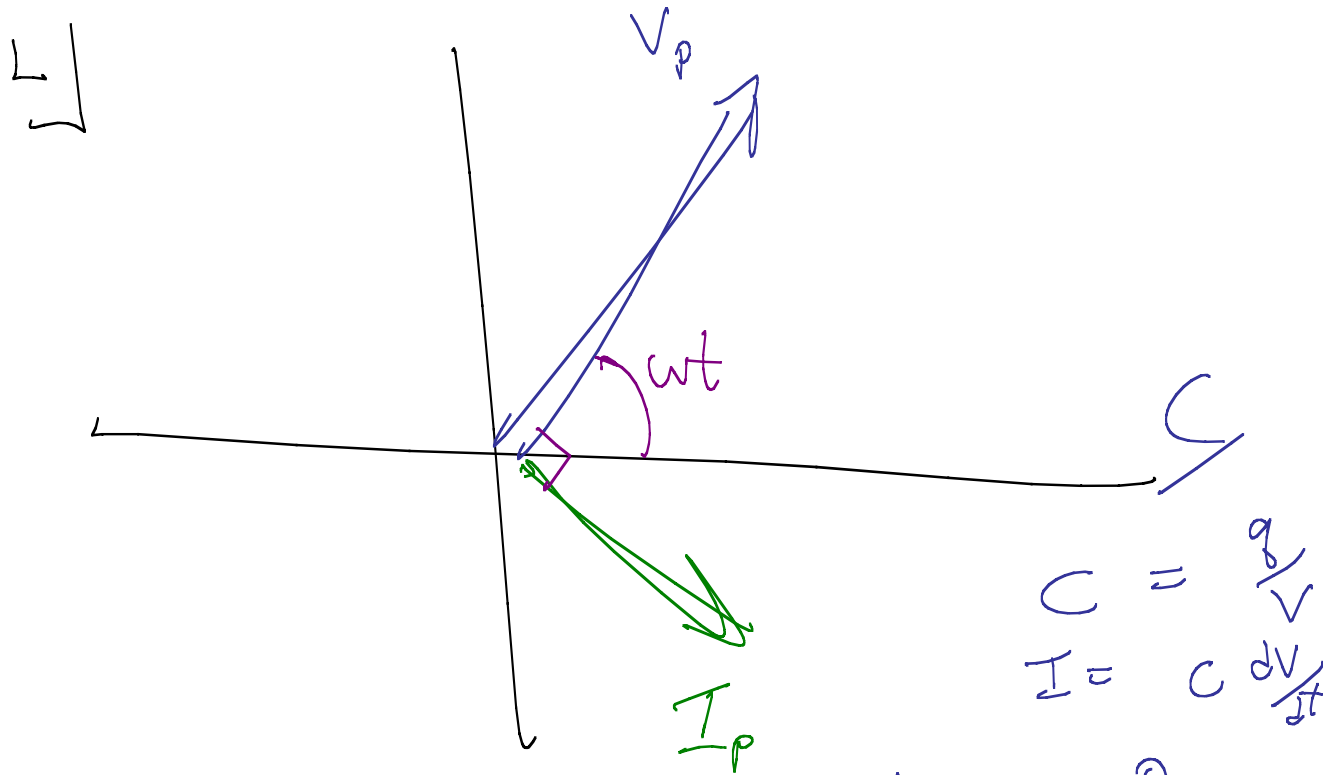

$$I = \frac{V_p}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

$I_p$

$X_L = \omega L$



$$L = \Phi_B / I$$

$$\mathcal{E} = -L \frac{dI}{dt}$$

$\omega \rightarrow 0$       Open  
 $\omega \rightarrow \infty$     Short


Short  
 Open

LC


Charge up capacitor  
to C

Close switch.


p. 497

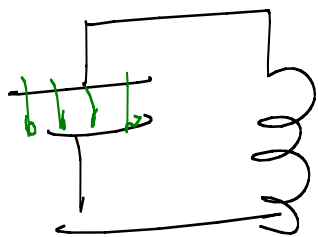

E in E field

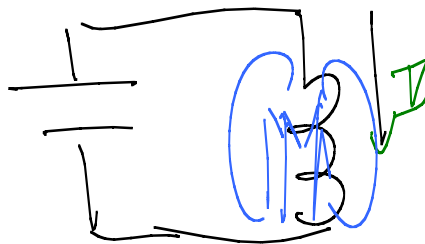

E in B field

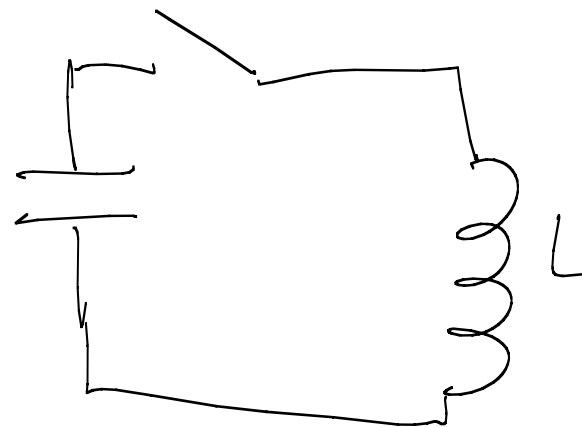

$$\frac{1}{2} CV^2$$


$$\frac{1}{2} LI^2$$



Energy goes between electric, magnetic

Capacitor corresponds to spring

Inductor corresponds to KE

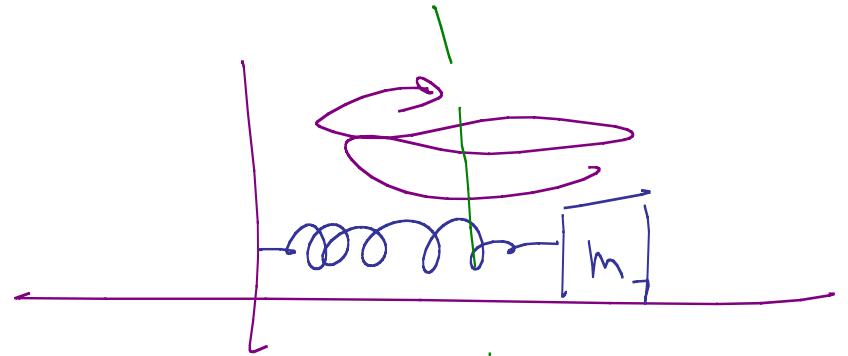

Inertia.

Use Gauss's E show something: LC circuit

$$U = U_B + U_E = \frac{1}{2} L I^2 + \frac{1}{2} C V^2$$

$$\text{Take } dU/dt = \text{constant}$$

$$\frac{1}{2} m v^2 \quad | \quad \frac{1}{2} L i^2$$

$$V = \Phi / C$$

$$I = dq/dt$$

$$\frac{dU}{dt} = L I \frac{dI}{dt} + C V \frac{dV}{dt} = 0 \quad V = \frac{q}{C}$$

Can show



$$L \frac{d^2 q}{dt^2} + \frac{1}{C} q = 0$$

$$\begin{aligned} \frac{dV}{dt} &= \frac{1}{C} \frac{dI}{dt} \\ &= \frac{1}{C} I \end{aligned}$$

$$\frac{d^2 q}{dt^2} = - \left( \frac{1}{LC} \right) q$$

$$\omega = \frac{1}{\sqrt{LC}}$$

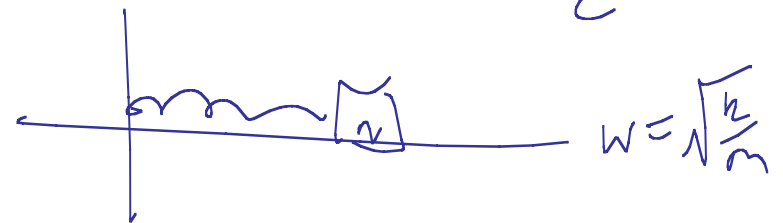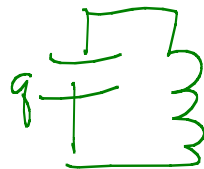$\omega^2 \swarrow$   
Ang. freq of osc's.



$$\frac{d^2 x}{dt^2} = - (\omega^2) x$$

$$q(t) = q_p \cos \omega t$$

$$\omega = \frac{1}{\sqrt{LC}} \quad \text{Resonant frequency}$$

28.24 Find the resonant freq. of an  
 LC circuit consisting of a  $0.22 \mu\text{F}$  cap  
 & a  $1.7 \text{ mH}$  inductor

$$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1.7 \times 10^{-3})(0.22 \times 10^{-6})}} = 5.2 \times 10^4 \text{ s}^{-1}$$



$$f = \frac{\omega}{2\pi} = 8.2 \text{ kHz}$$

28.25 An LC circuit with  $C = 18 \text{ mF}$  undergoes  
 oscillations w/ period  $2.4 \text{ s}$  Find inductance

$$f = \frac{1}{2.4 \text{ s}} = 0.42 \text{ Hz} \quad \omega = 2\pi f = 2.62 \text{ s}^{-1}$$

$$\omega = \frac{1}{\sqrt{LC}}$$
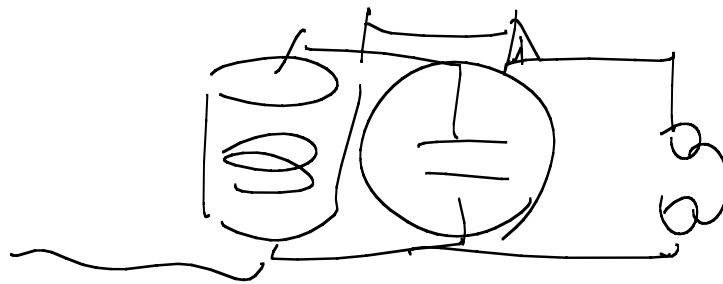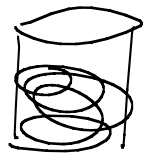
$$L = \frac{1}{\omega^2 C} = 8.1 \text{ H}$$



$$f = \begin{cases} 550 \text{ kHz} \\ 1600 \text{ kHz} \end{cases}$$

Rate Energy loss  $-I^2 R$



$$-I^2 R = \frac{d}{dt} \left( \frac{1}{2} L I^2 + \frac{1}{2} C V^2 \right)$$

Can show

$$L \frac{d^2 q}{dt^2} + R \frac{dq}{dt} + \frac{q}{C} = 0 \quad \omega = \frac{1}{\sqrt{LC}}$$

$$q(t) = q_0 e^{-Rt/2L} \cos \omega t$$

Damping

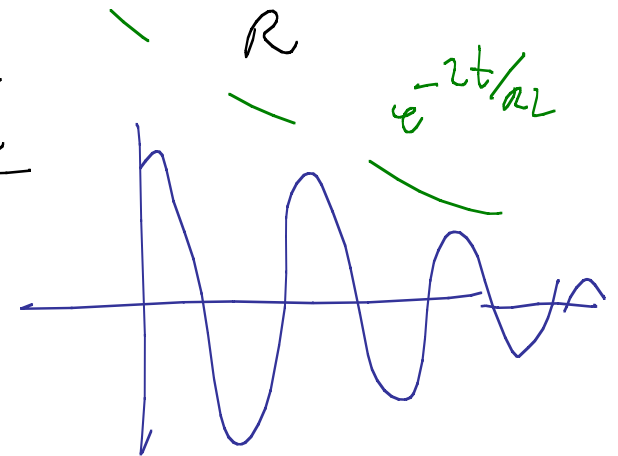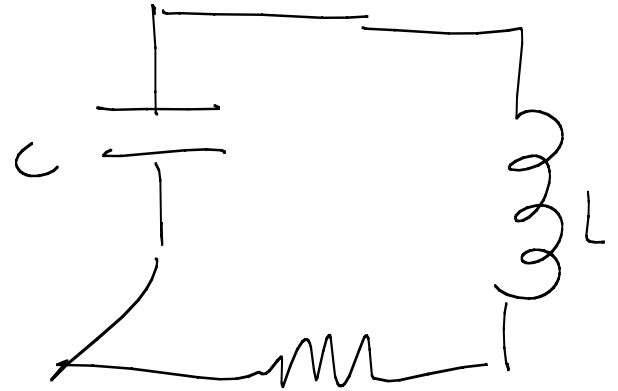


Time const  $\frac{2L}{R}$


If  $\frac{2L}{R} \approx \pi \tau_c$  or less critical damping

Analogy for previous


$$R \frac{d\dot{q}}{dt} \approx Rv$$

Friction. Velocity-dep. friction,

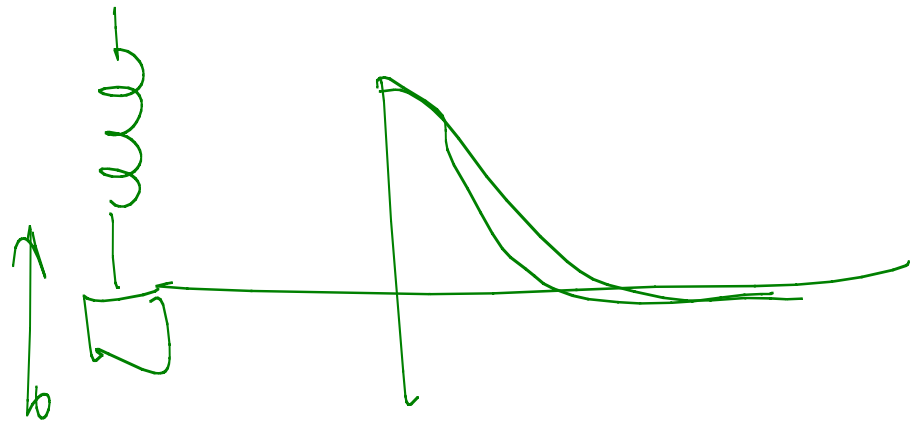

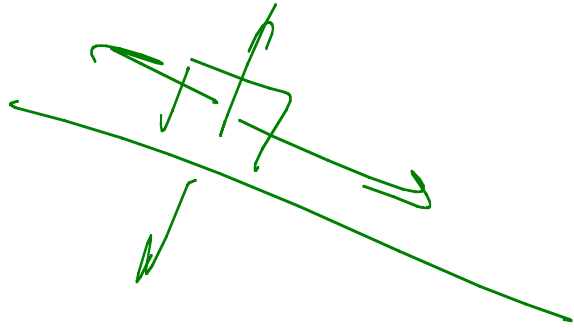

$$R \frac{dq}{dt}$$

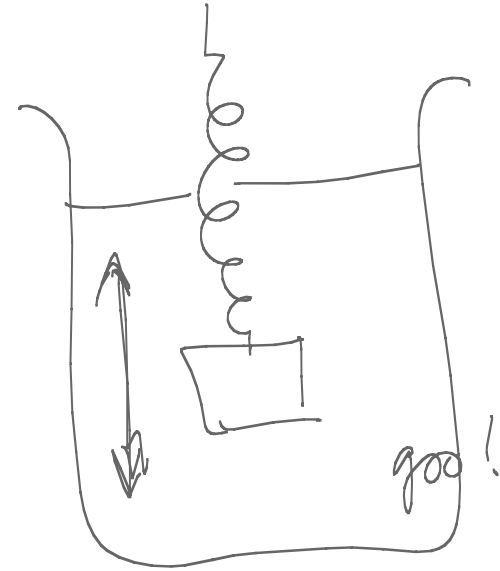

Analogy RLC circuit

Mass, spring, good!

$$f_k = \textcircled{-bv}$$