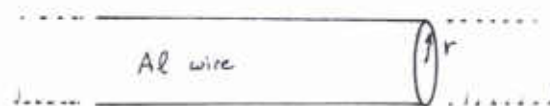


Name _____

Phys 122 — Section 4

Quiz #2

1. An conductor made of aluminum has a circular cross-section with radius 3.2 mm.



$$r = 3.2 \text{ mm}$$

a) What is the cross-sectional area of the conductor?

$$A = \pi r^2 = \pi (3.2 \times 10^{-3} \text{ m})^2 = 3.2 \times 10^{-5} \text{ m}^2$$

b) What length of the conductor has a resistance of 1.0Ω ? (The resistivity of Aluminum is $2.82 \times 10^{-8} \Omega \cdot \text{m}$.)

Use $R = \rho \frac{l}{A}$, find l :


$$l = \frac{AR}{\rho} = \frac{(3.2 \times 10^{-5} \text{ m}^2)(1.0 \Omega)}{(2.82 \times 10^{-8} \Omega \cdot \text{m})} = 1.1 \times 10^3 \text{ m} = 1.1 \text{ km}$$

2. A $1.5 \text{ k}\Omega$ resistor is connected to a 12.0 V battery.

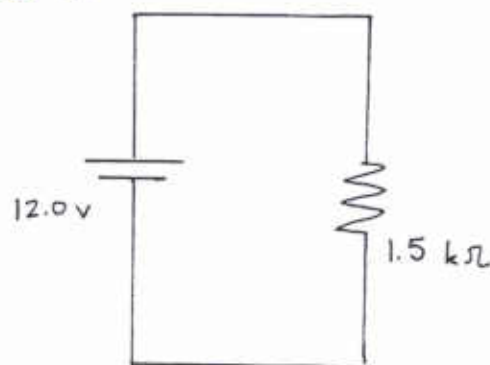a) What current flows through the resistor?

Ohm's Law:

$$I = \frac{V}{R} = \frac{12.0 \text{ V}}{1.5 \times 10^3 \Omega} = 8.0 \times 10^{-3} \text{ A} = 8.0 \text{ mA}$$



b) How much energy is dissipated in the resistor in 1.0 hour?


Power dissipated in resistor is


$$P = I^2 R = (8.0 \times 10^{-3} \text{ A})^2 (1.5 \times 10^3 \Omega) = 9.6 \times 10^{-2} \text{ W}$$

In one hour = 3600 s, the energy dissipated is


$$\text{Energy} = Pt = (9.6 \times 10^{-2} \text{ W})(3600 \text{ s}) = 346 \text{ J}$$

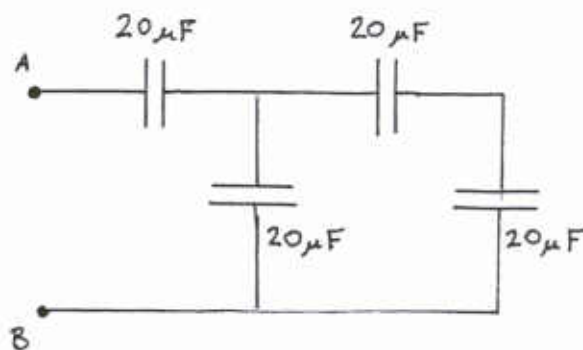3. Find the equivalent capacitance (i.e. the capacitance between points A and B) for the combination shown here.




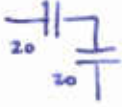The farthest two capacitors : 
are in series; they reduce
to: $\frac{1}{C_{\text{ser}}} = \frac{1}{20\mu\text{F}} + \frac{1}{20\mu\text{F}}$

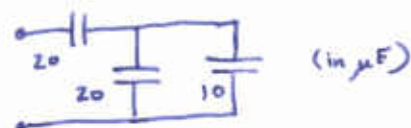→ $C_{\text{ser}} = 10\mu\text{F}$. The combination is now:



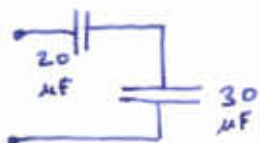for the $10\mu\text{F}$ and $20\mu\text{F}$ cap's are in
parallel, giving:



Finally, combine the

series $20\mu\text{F}$ and $30\mu\text{F}$ cap's to get:

$$\frac{1}{C_{\text{eq}}} = \frac{1}{20\mu\text{F}} + \frac{1}{30\mu\text{F}} \rightarrow \boxed{12\mu\text{F}}$$

You must show all your work!

$$I = \frac{q}{t} \quad V = IR \quad R = \rho \frac{\ell}{A} \quad P = VI = I^2 R = \frac{V^2}{R} \quad q = CV \quad \text{Energy} = Pt$$

$$R_{\text{ser}} = R_1 + R_2 + \dots \quad \frac{1}{R_{\text{par}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots \quad \frac{1}{C_{\text{par}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots \quad C_{\text{par}} = C_1 + C_2 + \dots$$

$$\text{Circle: } C = 2\pi R \quad A = \pi R^2 \quad \text{Sphere: } A = 4\pi R^2 \quad V = \frac{4}{3}\pi R^3$$

$$V_{\text{rms}} = \frac{V_0}{\sqrt{2}} \quad I_{\text{rms}} = \frac{I_0}{\sqrt{2}}$$

Some EM units: Coulomb, Volt, Farad, Ampere, Watt, Ohm

Sum of currents going into junction equals sum of currents coming out of junction; around any closed loop, the sum of potential gains equals the sum of potential drops.