

Phys 2120-4 10/1/12

Note Title

10/1/2012

Electric Circuits

Kirchhoff Rules !!

Apply rules until
you have enough
indep't. eqns.

Junction $\sum I_{in} = \sum I_{out}$

Loop: Sum up all voltage
drops & gains $= 0$

Assign currents to each
branch

25.25


Basic eqns

Junctions:

$$-I_1 + I_2 + I_3 = 0$$

$$+6V - (2\Omega) I_1 - (1\Omega) I_3 = 0$$
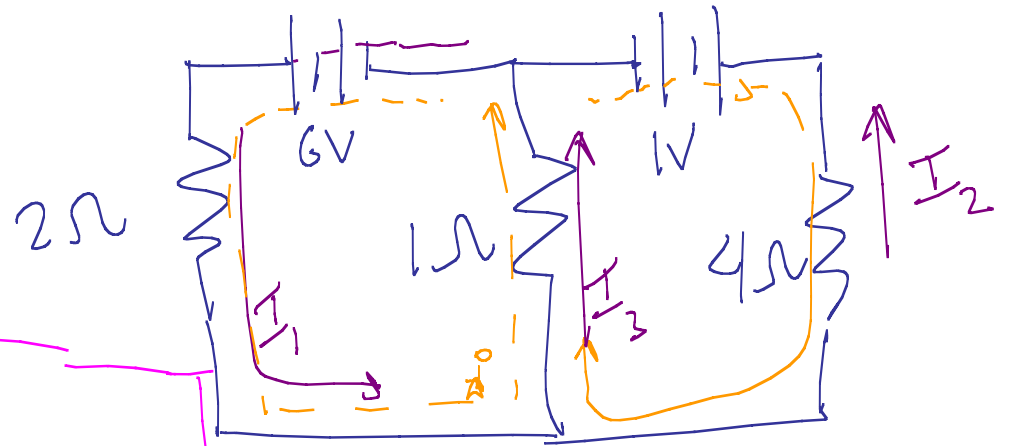
$$1V + (4\Omega) I_2 - (1\Omega) I_3 = 0$$



Set of
linear equations
3x3

p. 427

Sub'd

$$6V - 3I_1 + I_2 = 0$$

Add & subtract

$$1V + 5I_2 - I_1 = 0$$

$$I_2 = 0.214 A$$

$$I_1 = 2.07 A$$


$$I_3 = 1.86 A$$

More stuff


Measurements of quantities

Ammeters & Voltmeter


Current

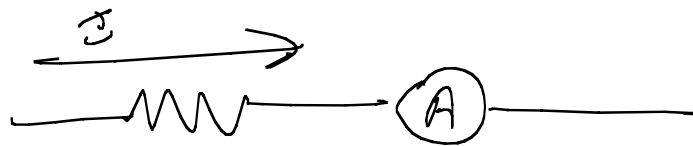


Voltmeter

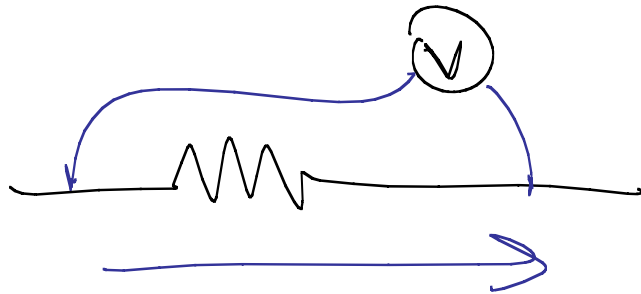

Reads out potential diff.

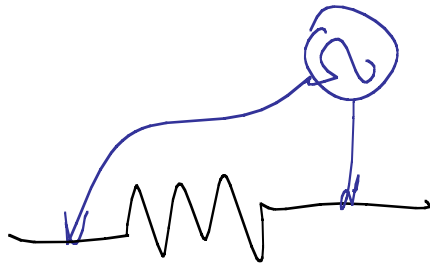


Ohmmeter

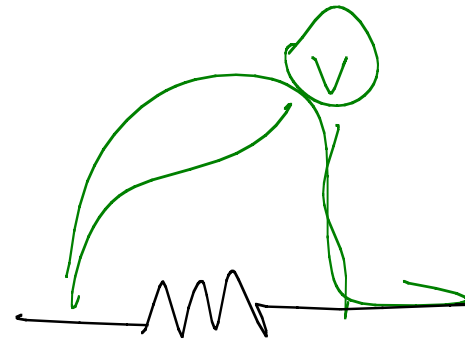


Low resistance

Capacitor in Circuit

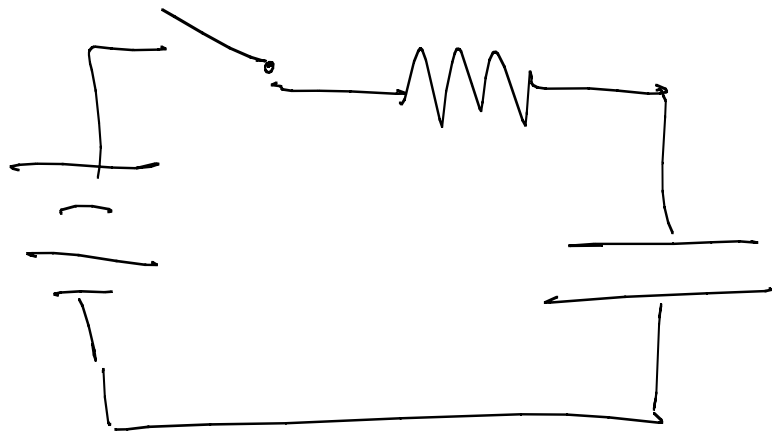


I big initially
eventually dies off

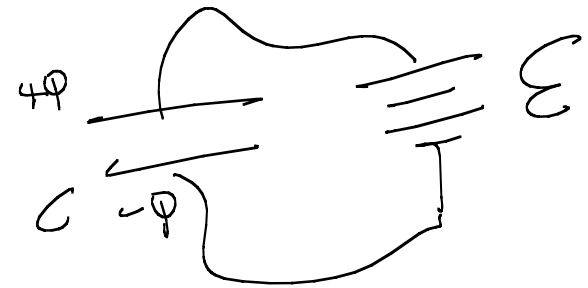


$$C \epsilon = Q$$

Close switch,

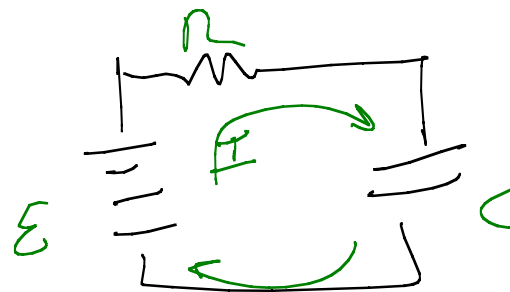



Eventually,
charged

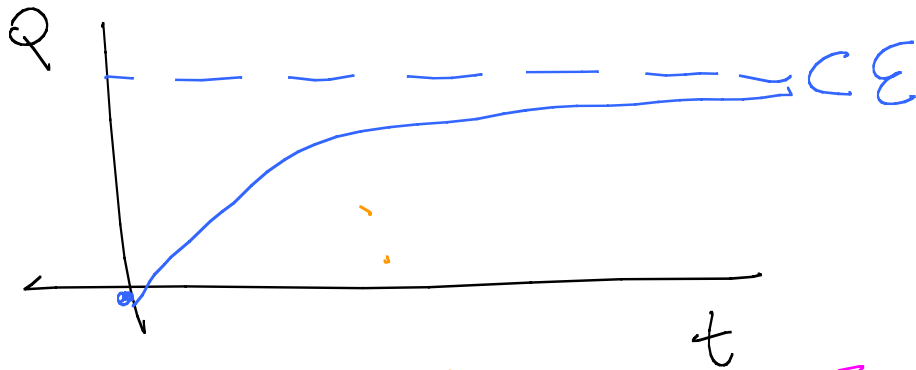

$$\mathcal{E} - IR - \frac{Q}{C} = 0$$

$I(t) \quad Q(t)$

Take deriv.

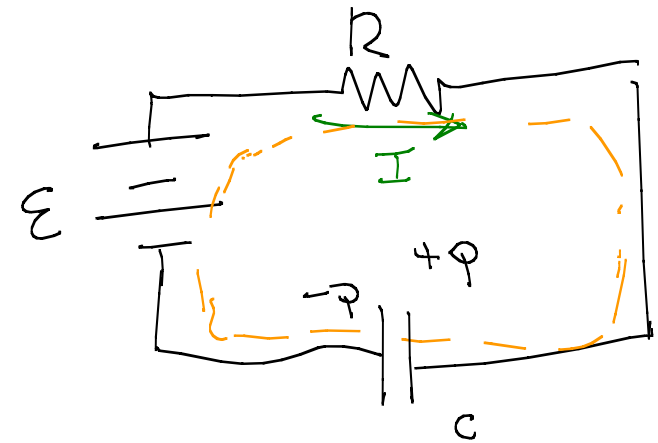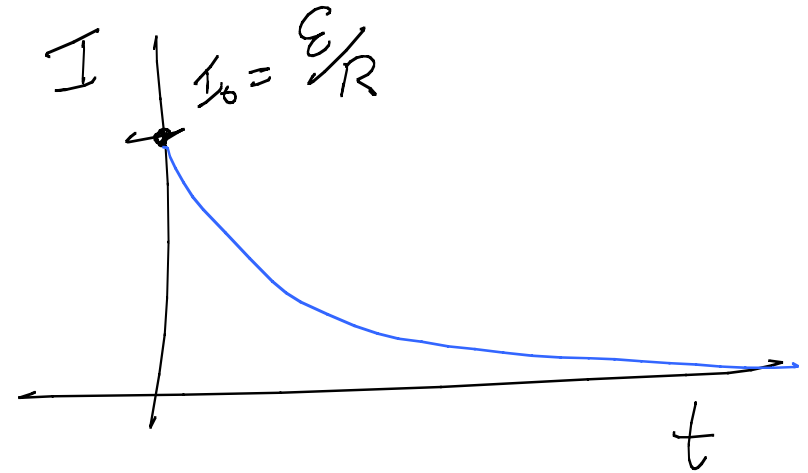

$$- \frac{dI}{dt} R - \frac{1}{C} I = 0$$

$$\frac{dQ}{dt} = I$$

$$\frac{dI}{dt} = -\frac{1}{RC} I$$


$$I = I_0 e^{-t/RC}$$

$$I_0 = \frac{\mathcal{E}}{R}$$

$$I = \frac{\mathcal{E}}{R} e^{-t/RC}$$


$$V_C = \frac{Q}{C} = \mathcal{E} - IR$$

$$= \mathcal{E} (1 - e^{-t/RC})$$

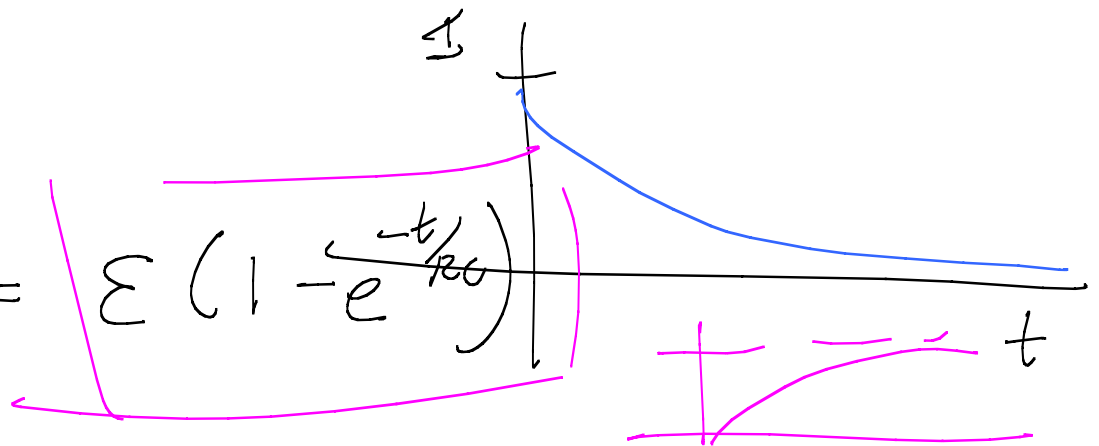

$$I = I_0 e^{-t/RC}$$

$$= I_0 e^{-t/\tau}$$

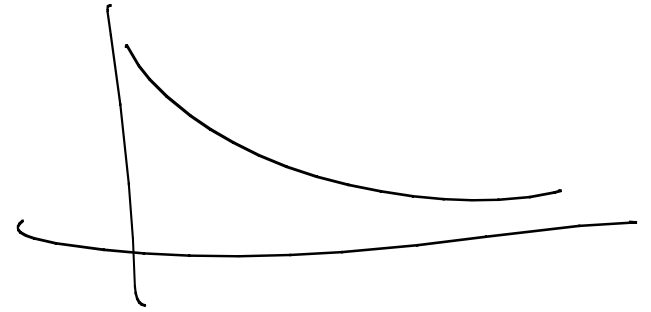

$$\tau = RC \quad \text{time constant}$$

$$e^{-t/\tau}$$

of RC circuit

t small, product is ≈ 1
 t comp'd to τ

t large comp'd to τ ^{exp is} small

25.31 Show that RC has units of time seconds?

$$[RC] = \frac{\cancel{\text{Volt}}}{\text{Amp}} \cdot \frac{\text{Coul}}{\cancel{\text{Volt}}} = \frac{\cancel{\text{Coul}}}{\cancel{\text{Coul}}/\text{sec}} = \text{sec}$$


Ohm's Law $Q = CV$

$V = IR$

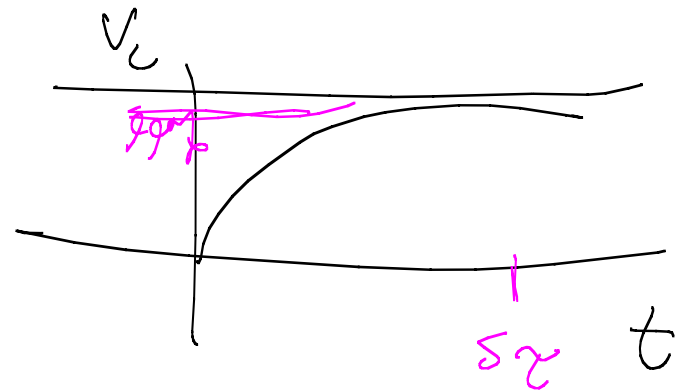25.33 Show that a capacitor is charged to approx. 99% of applied voltage in 5 time constants

$$V_c = \mathcal{E} (1 - e^{-t/RC})$$

$$\underline{Q_c} = V_c C = \underline{C\mathcal{E}} (1 - e^{-t/RC})$$



When is $V_c = 99\% \mathcal{E}$?

$$\cancel{\mathcal{E}} (1 - e^{-t/RC}) = 0.99 \cancel{\mathcal{E}}$$

$$0.01 = e^{-t/RC}$$

$$-t/RC = -4.6$$

$$t = (4.6) RC$$