

Name \_\_\_\_\_

Units?  
Units?

Feb. 16, 2004

Phys 2020  
Quiz #2 — Spring 2004


1. A 12.0 V potential difference is applied across the plates of a  $6.00 \mu\text{F}$  capacitor.

a) What is charge stored on the capacitor?

Use  $q = CV$ , then:

$$q = CV = (6.00 \times 10^{-6} \text{ F})(12.0 \text{ V})$$
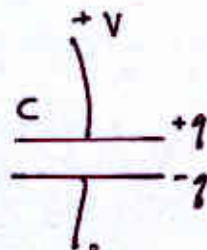
$$= \boxed{7.20 \times 10^{-5} \text{ C}} = 72.0 \mu\text{C}$$




b) How much energy is stored in the capacitor?

Energy stored in capacitor is  $E = \frac{1}{2} CV^2$ , so:

$$\text{Energy} = \frac{1}{2} CV^2 = \frac{1}{2} (6.00 \times 10^{-6} \text{ F})(12.0 \text{ V})^2 = \boxed{4.32 \times 10^{-4} \text{ J}}$$

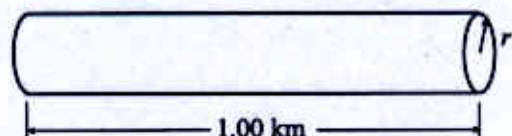2. What is the resistance of a 1.00 km length of aluminum wire which has a circular cross-section with a radius of 1.00 mm?

The resistivity of aluminum is  $2.75 \times 10^{-8} \Omega \cdot \text{m}$ .



Use  $R = \rho \frac{L}{A}$ . Since cross-sectional area is

$$A = \pi r^2 = \pi (1.00 \times 10^{-3} \text{ m})^2 = 3.14 \times 10^{-6} \text{ m}^2$$

then the resistance is

$$R = \rho \frac{L}{A} = (2.75 \times 10^{-8} \Omega \cdot \text{m}) \frac{(1.00 \times 10^3 \text{ m})}{(3.14 \times 10^{-6} \text{ m}^2)}$$

$$= \boxed{8.75 \Omega}$$

3. An electric circuit, shown at the right, consists of a 12.0 V battery connected to two resistors ( $150\ \Omega$  and  $250\ \Omega$ ) connected in series.


a) Find the current in the circuit.

Equivalent resistance is

$$R_{eq} = R_1 + R_2 = 150\ \Omega + 250\ \Omega = 400\ \Omega$$

Then from  $V = IR_{eq}$ , we have
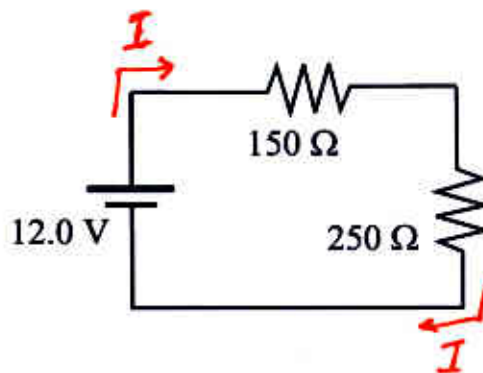
$$I = V/R_{eq} = 12.0\text{V}/400\ \Omega = \boxed{3.00 \times 10^{-2}\text{ A}} = 30.0\text{ mA}$$



b) What is the potential difference (drop) across the  $250\ \Omega$  resistor?

current in that resistor is  $3.00 \times 10^{-2}\text{ A}$  so from Ohm's law,

$$V = IR = (3.00 \times 10^{-2}\text{ A})(250\ \Omega) = \boxed{7.50\text{ V}}$$

c) At what rate is energy dissipated in the  $150\ \Omega$  resistor?

Rate of energy dissipation is  $P = I^2 R$ . Current in  $150\ \Omega$  resistor is also  $3.00 \times 10^{-2}\text{ A}$ , so

$$P = I^2 R = (3.00 \times 10^{-2}\text{ A})^2 (150\ \Omega) = \boxed{0.135\text{ W}}$$

---

**You must show all your work and include the right units with your answers!**

$$k = \frac{1}{4\pi\epsilon_0} \quad \epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N}\cdot\text{m}^2} \quad m_{\text{elec}} = 9.1094 \times 10^{-31} \text{ kg} \quad e = 1.602 \times 10^{-19} \text{ C}$$

$$\Delta E_{\text{PE}} = q_0 \Delta V \quad V_{\text{pt-ch}} = k \frac{q}{r} \quad E_x = -\frac{\Delta V}{\Delta x} \quad 1 \text{ eV} = 1.602 \times 10^{-19} \text{ J}$$

$$A = \pi R^2 \quad q = CV \quad C_{\text{air}} = \frac{\epsilon_0 A}{d} \quad C_{\text{diel}} = \kappa C_{\text{air}} \quad \text{Energy} = \frac{q^2}{2C} = \frac{1}{2} CV^2$$

$$V = IR \quad R = \rho \frac{L}{A} \quad R_{\text{ser}} = R_1 + R_2 + \dots \quad \frac{1}{R_{\text{par}}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$P = VI = I^2 R = \frac{V^2}{R} \quad \text{Energy} = Pt \quad 1 \text{ eV} = 1.602 \times 10^{-19} \text{ J}$$