

Phys 2120-4 10/31/12



Note Title

10/31/2012

AC Circuits


$$\omega = 2\pi f$$

c)

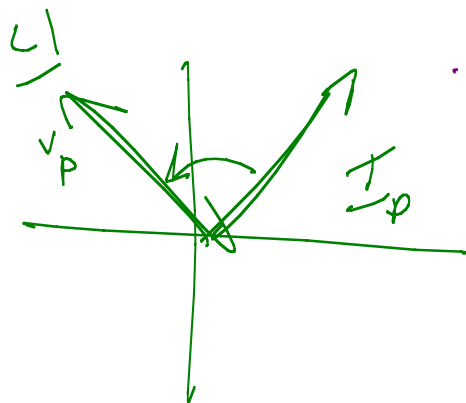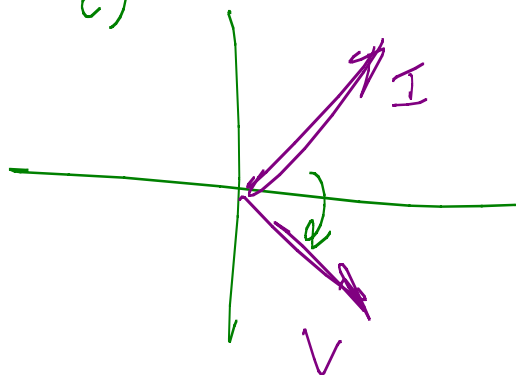

phasors


p. 495

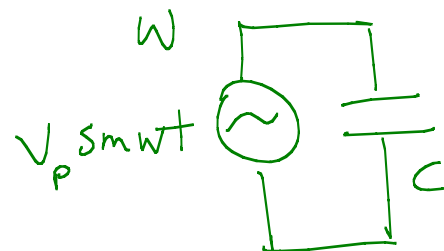

$$V_p = I_p X_c$$


$$X_c = \frac{1}{\omega C}$$

Ohms

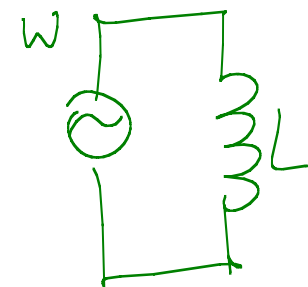

$$V_p = I_p X_L$$

$$X_L = \omega L$$

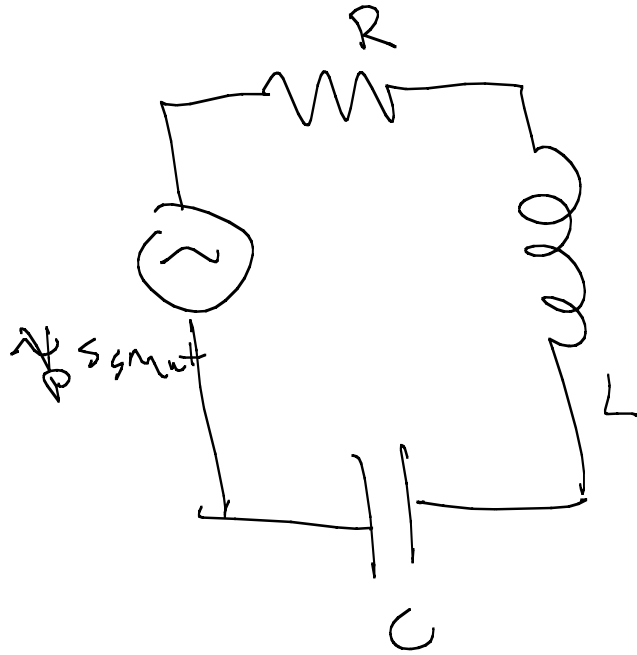

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


Mech. analogy.

Current(s), Voltages,
Phases

Current oscillates



Same for all elements

$$I(t) = I_p \sin(\omega t)$$

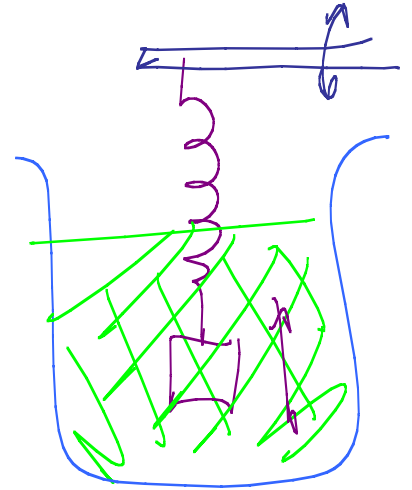

In the inductor, V leads
the current

In the capacitor,
 I leads V
 V lags I

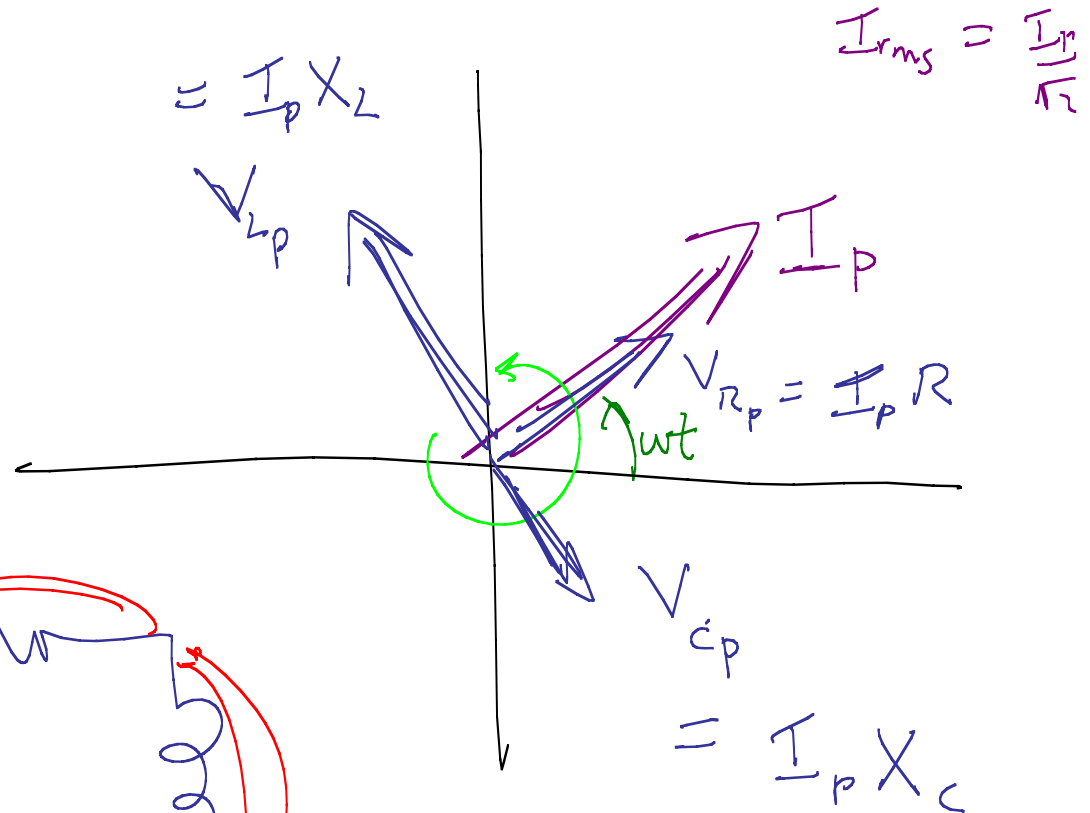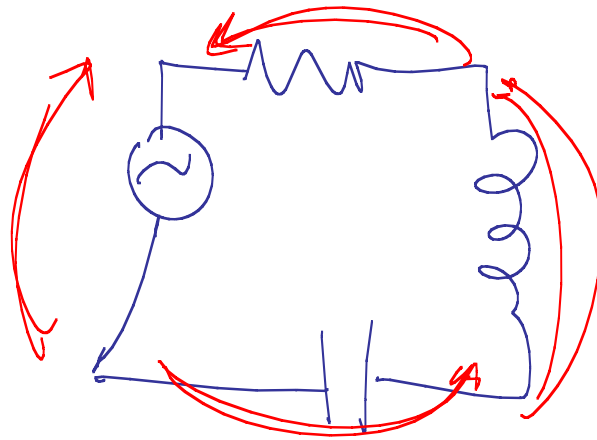


$$V_p = \sqrt{V_{R_p}^2 + (V_{L_p} - V_{C_p})^2}$$

pitch
across
gen

$$= \sqrt{(\underline{I}_p R)^2 - (\underline{I}_p X_L - \underline{I}_p X_C)^2}$$


$$= \underline{I}_p \sqrt{R^2 + (X_L - X_C)^2}$$
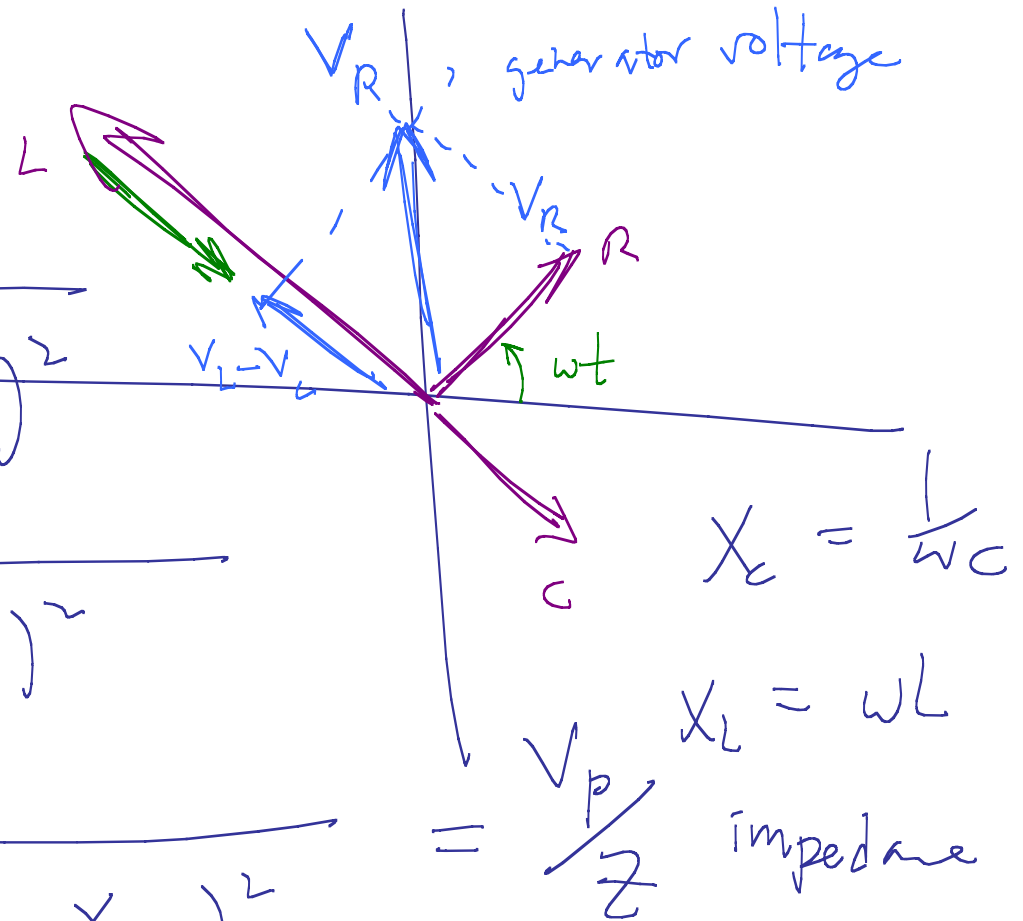
$$\underline{I}_p = \frac{V_p}{\sqrt{R^2 + (X_L - X_C)^2}}$$



Special cases

$$X_L = X_C$$

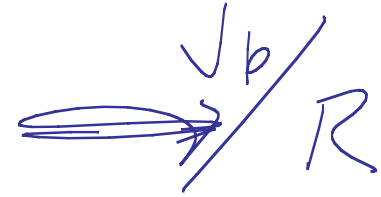


Then I_p is
biggest.

Resonance

$$\omega L = \frac{1}{\omega C}$$


$$\omega^2 = \frac{1}{LC}$$
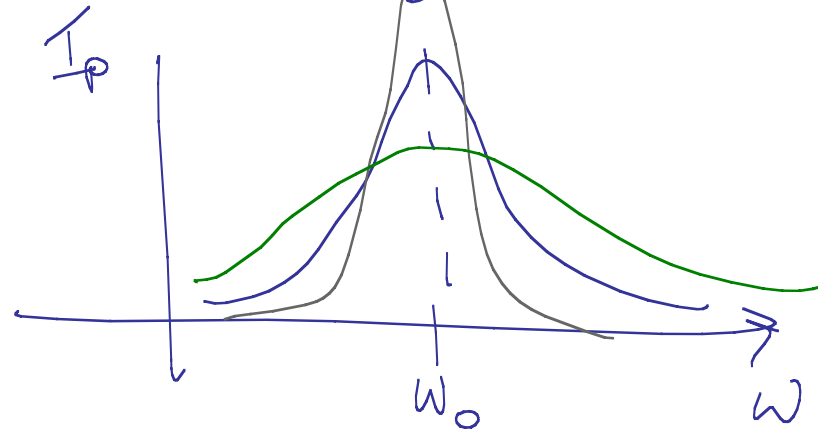
$$\omega = \frac{1}{\sqrt{LC}} = \omega_0$$



p. 501

Q-value

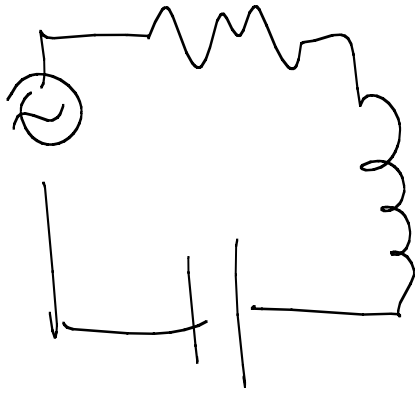

ϕ = phase angle


$$\tan \phi = \frac{X_L - X_C}{R}$$



$$= \frac{\omega L - \frac{1}{\omega C}}{R}$$

$$= \phi_v - \phi_i$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

= impedance

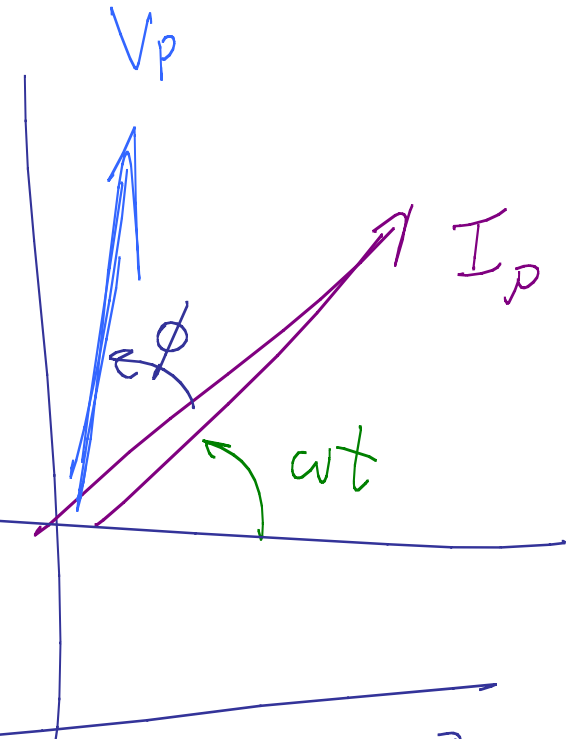

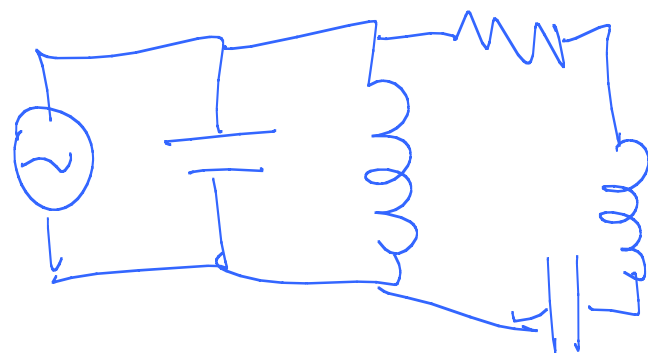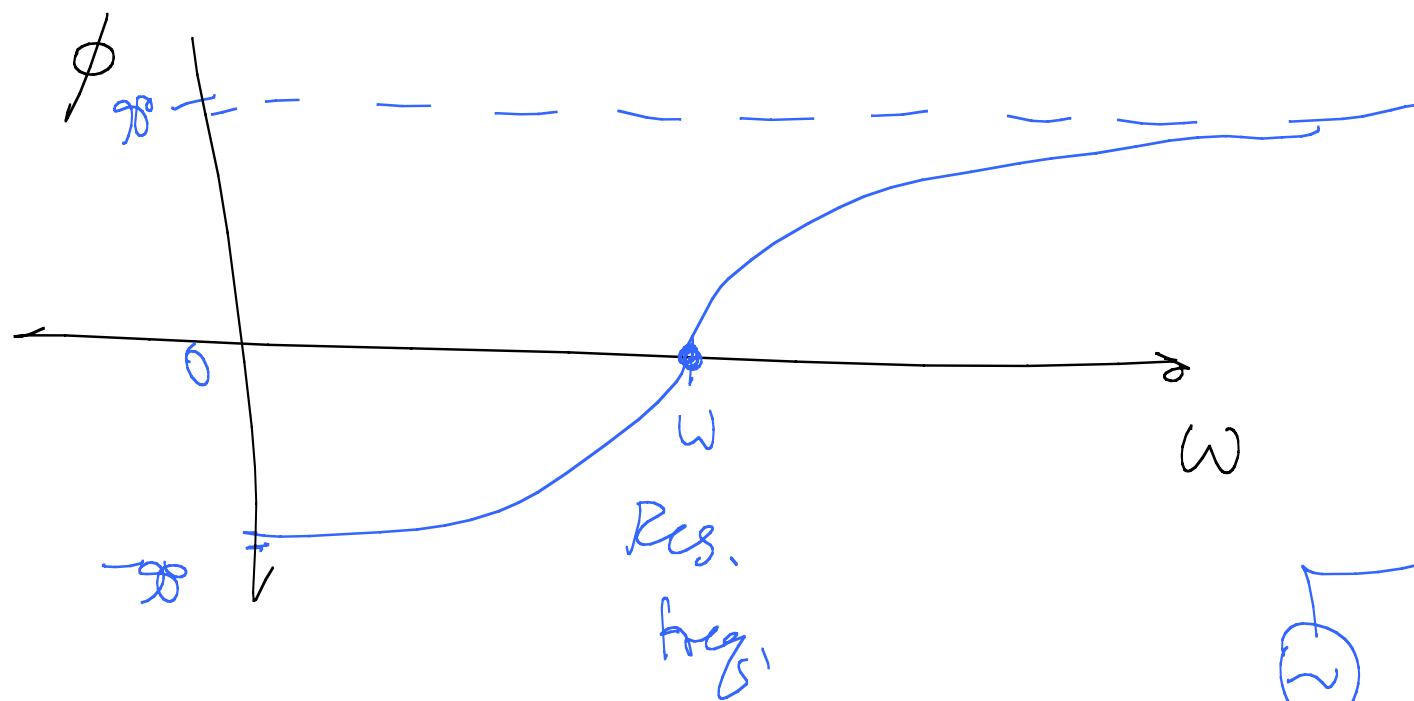

Power Energy loss (in R)
 $P = I^2 R$ instantaneously

$$P = V_R I$$
$$V_{R_p} = V_p \cos \phi$$
$$= V_p \cos \phi (\omega t + \phi) I_p \sin \omega t$$

