
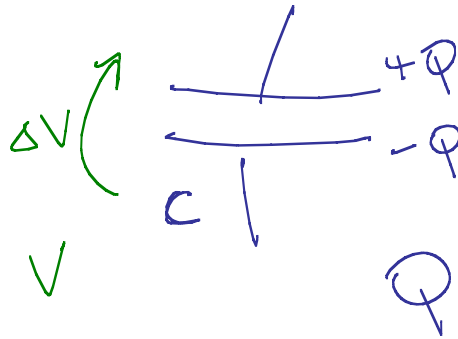


Capacitors

$$Q = CV$$

C in Farads

Combine capacitors

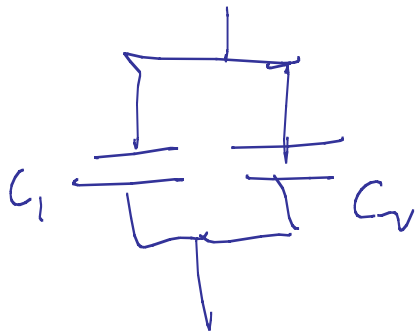

$$C_{eq} = C_1 + C_2$$

Energy stored
at potential V

$$U = \frac{1}{2} CV^2$$






$$\frac{1}{C_{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)$$

in general:

$$\frac{1}{C_{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \right)$$

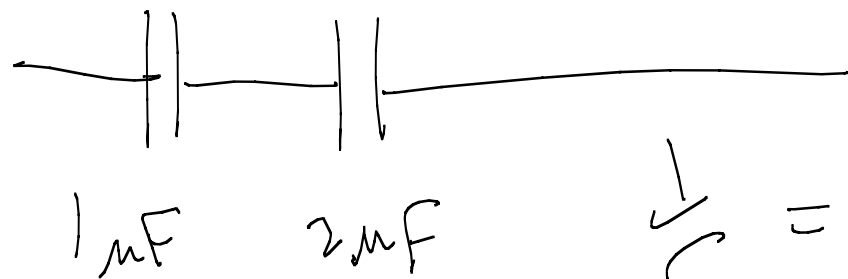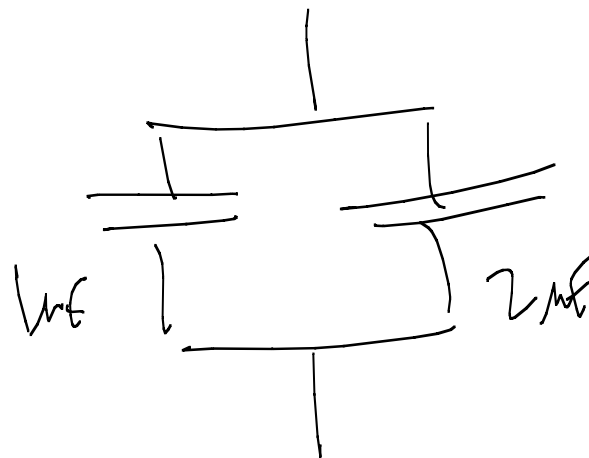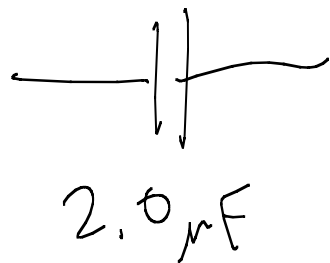23.29 You have a $1.0 \mu\text{F}$ and $2.0 \mu\text{F}$ capacitor.
 What cap. can you get by conn. in series
 or parallel?





$$\frac{1}{C_{eq}} = \left(\frac{1}{1 \mu\text{F}} + \frac{1}{2 \mu\text{F}} \right)$$

$$= 3 \mu\text{F}$$

$$C_{eq} = 0.667 \mu\text{F}$$

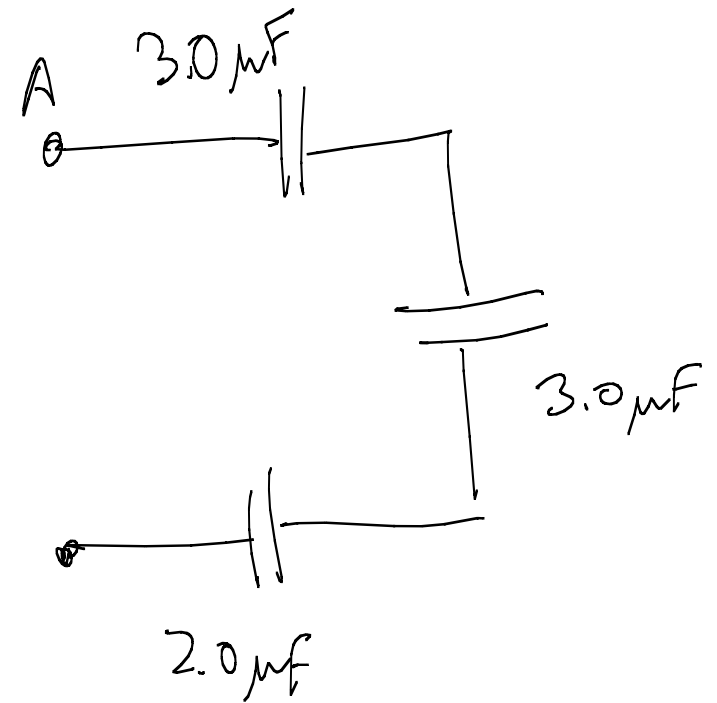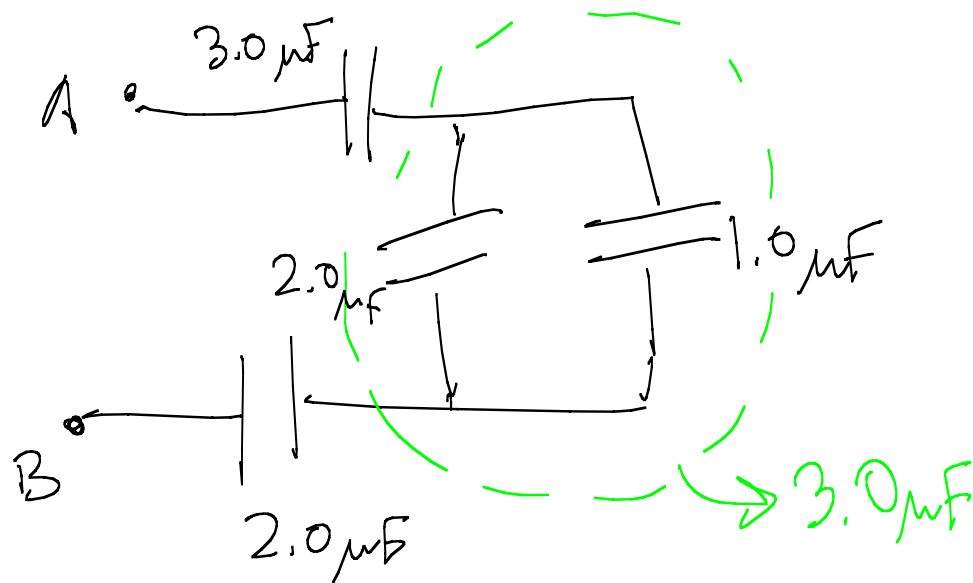23.51 What's the equivalent cap. measured between A and B:




Now, 3 in series

$$\frac{1}{C_{eq}} = \left(\frac{1}{3\mu F} + \frac{1}{3\mu F} + \frac{1}{2\mu F} \right)$$


$$C_{eq} = 0.86\mu F$$

Next problem

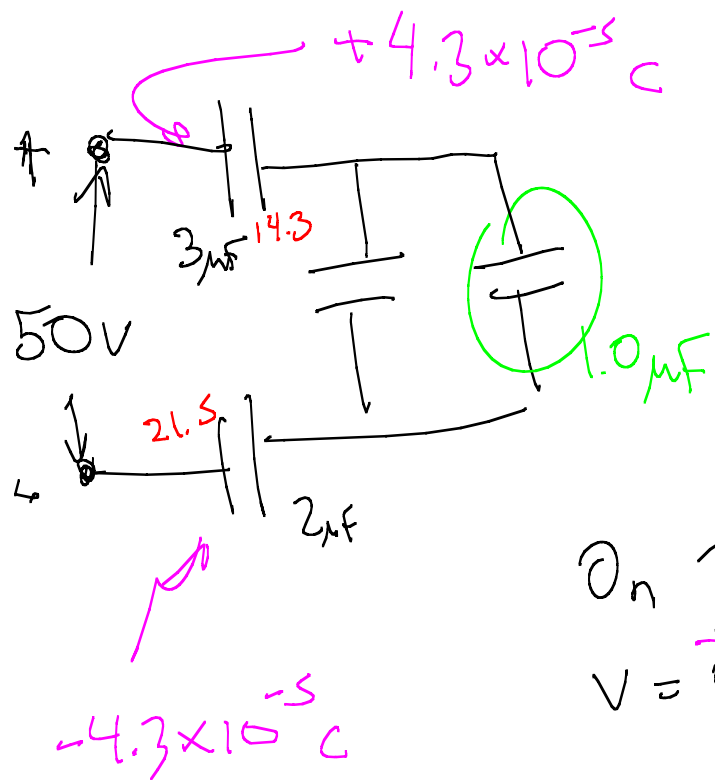23.52 In this config of cap's find the energy stored in the $1.0\mu F$ cap when a $50V$ battery is conn'd across A & B ?



$$U = \frac{1}{2} C V^2$$

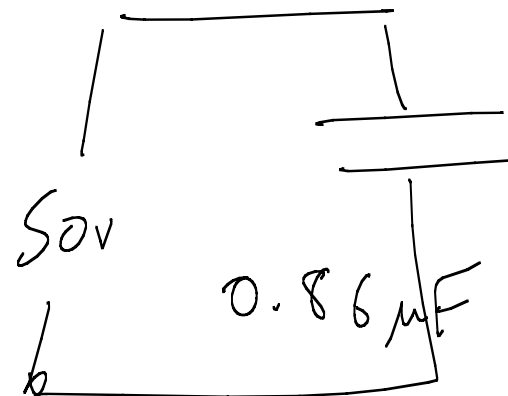

$$Q \text{ on } 3\mu\text{F}$$

$$V = \frac{Q}{C} = \frac{4.3 \times 10^{-5} \text{ C}}{3\mu\text{F}}$$

$$= 14.3 \text{ V}$$


$$Q = (50)(0.86\mu\text{F})$$

$$= 4.3 \times 10^{-5} \text{ C}$$

$$\text{On } 2\mu\text{C} \quad V = \frac{Q}{C} = \frac{4.3 \times 10^{-5} \text{ C}}{2\mu\text{F}} = 21.5 \text{ V}$$

Potential across the parallel pair is
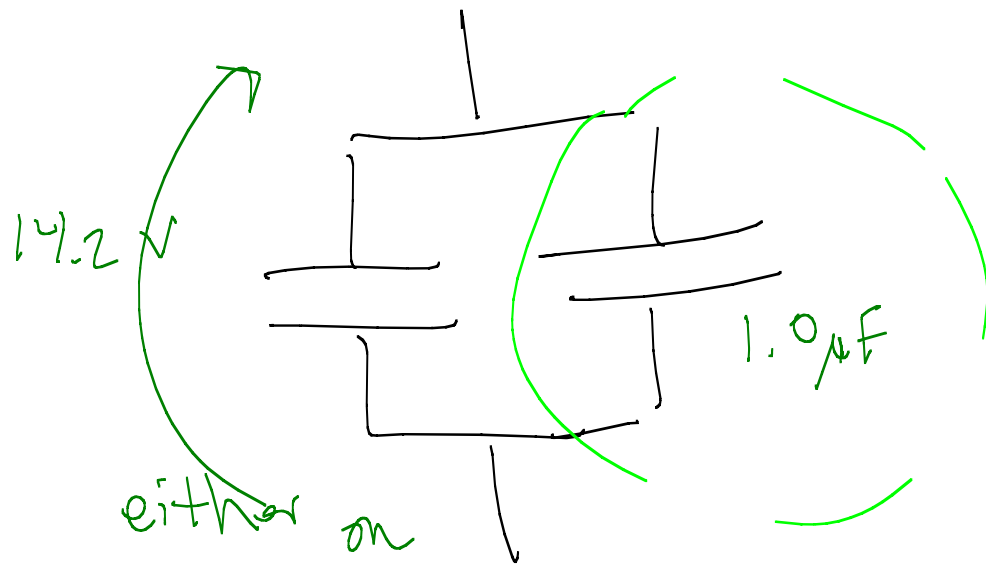
$$50\text{V} - 14.3 - 21.5 = 14.2\text{V}$$




$$U = \frac{1}{2} C V^2$$

$$= \frac{1}{2} (1.0 \mu\text{F}) (14.2\text{V})^2$$

$$= 1.0 \times 10^{-4} \text{ J}$$


$$= 100 \mu\text{J}$$

23.31

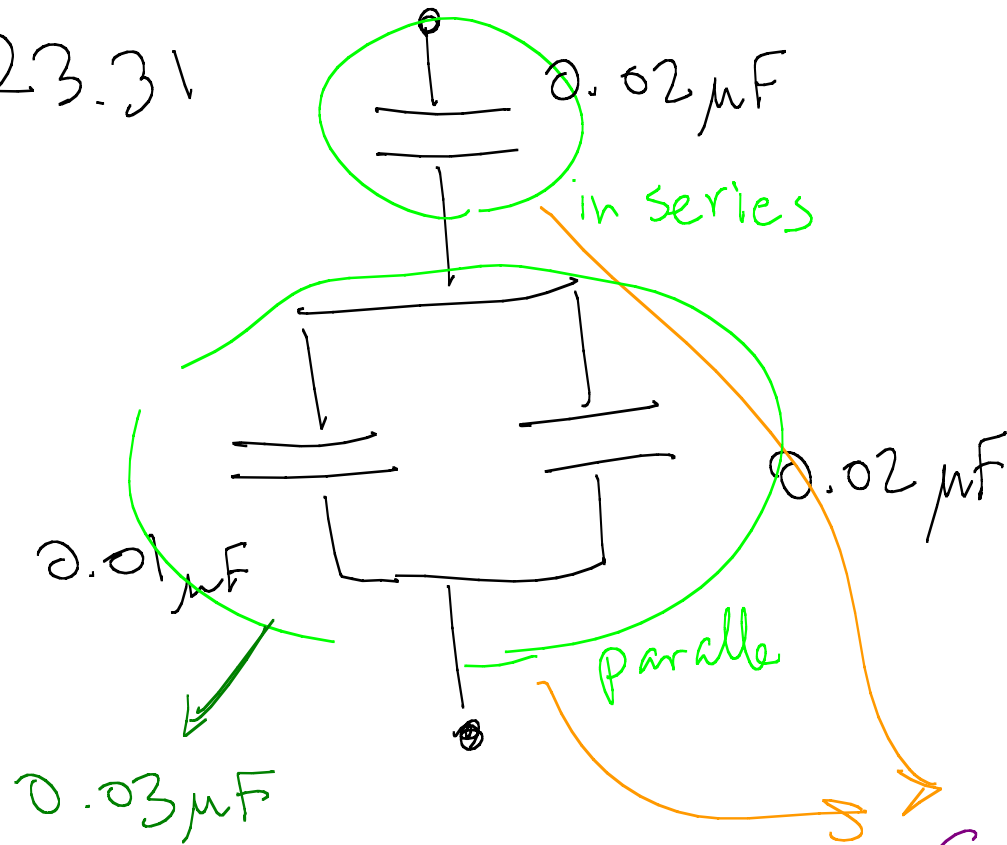

- Find C_{eq}
- Find charge & voltage on each cap when 100-V battery is connected across terminals.

$$C_{eq} = 0.012 \mu\text{F}$$

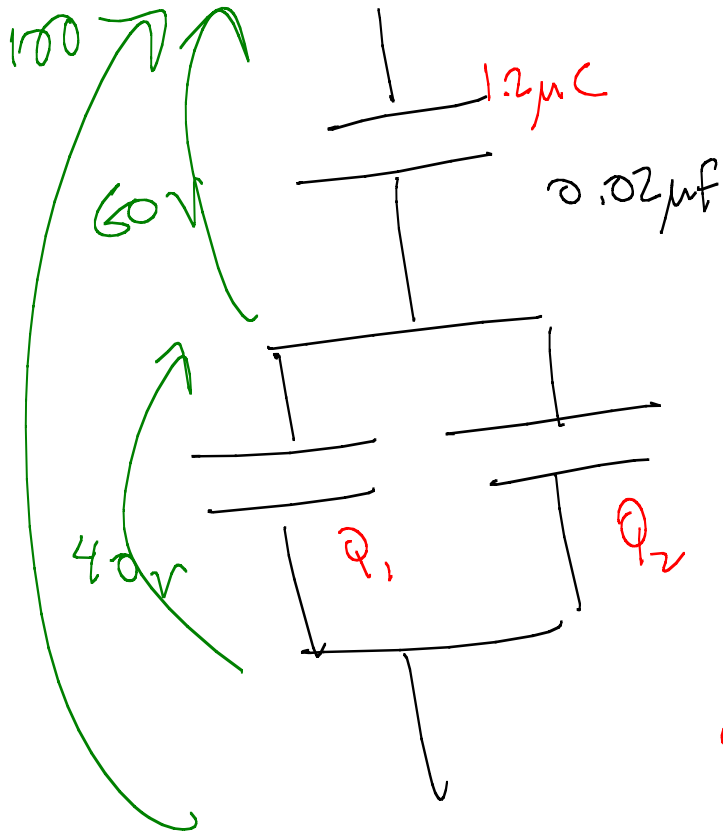

$$100\text{V} \quad C_{eq} = 0.012\mu\text{F}$$

$$Q = CV \quad Q = (0.012\mu\text{F})(100\text{V})$$

$$= 1.2\mu\text{C}$$

$$Q_1 + Q_2 = 1.2\mu\text{C}$$

On top capacitor

$$V = \frac{Q}{C} = 60\text{V}$$

$$= \frac{1.2\mu\text{C}}{0.02\mu\text{F}}$$

On the bottom two cap's

$$V_1, V_2 = 40 \text{ V}$$

$$Q_1 = C_1 V_1 = 0.4 \mu\text{C}$$

$$Q_2 = C_2 V_2 = 0.80 \mu\text{C}$$

$$(Q_1 + Q_2 = 1.2 \mu\text{C}) \quad /$$




Chap 24


Electric Current

Current is produced when we maintain a potential diff across conductor, allow charge to keep flowing

Pictures denote a fictitious positive current

Reality, neg. electrons move.

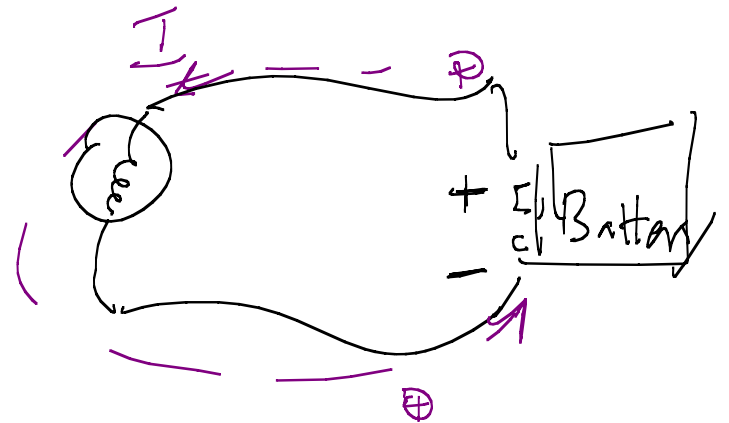

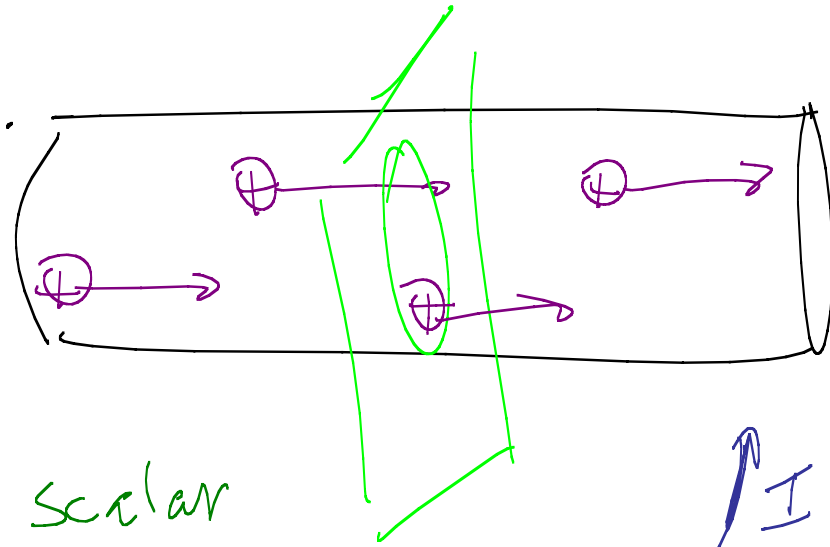


Measure charge per
time crossing plane.
→ current.

$$= \text{Elec. current} = \underline{I}$$


$$= \frac{Q}{t}$$

$$[I] = \frac{\text{Coulomb}}{\text{sec}}$$

$$= \text{Amp}$$

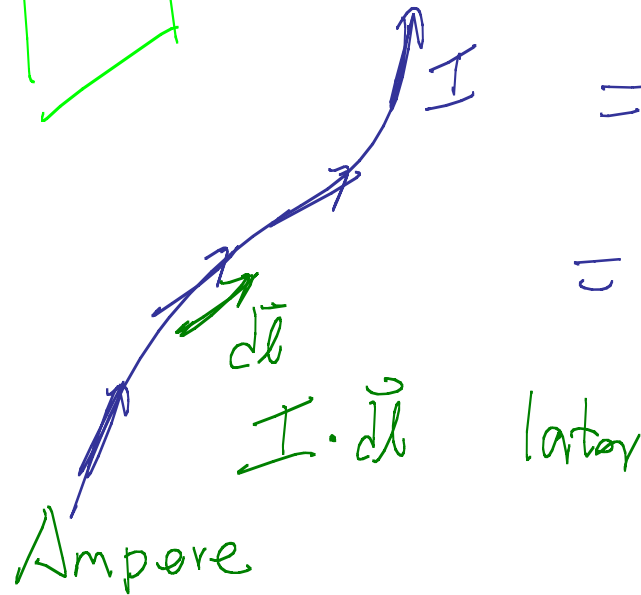


Ampere

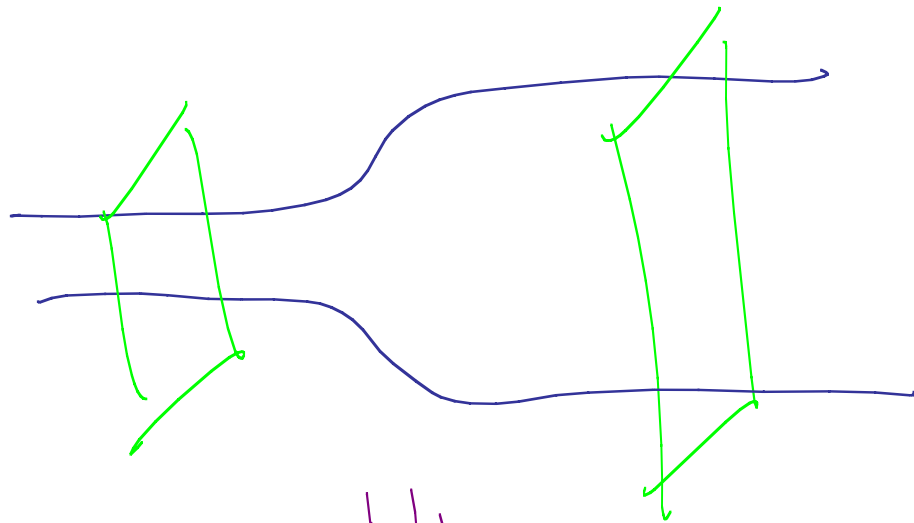


$$I = \frac{d\Phi}{dt}$$

I will be time-dep⁴

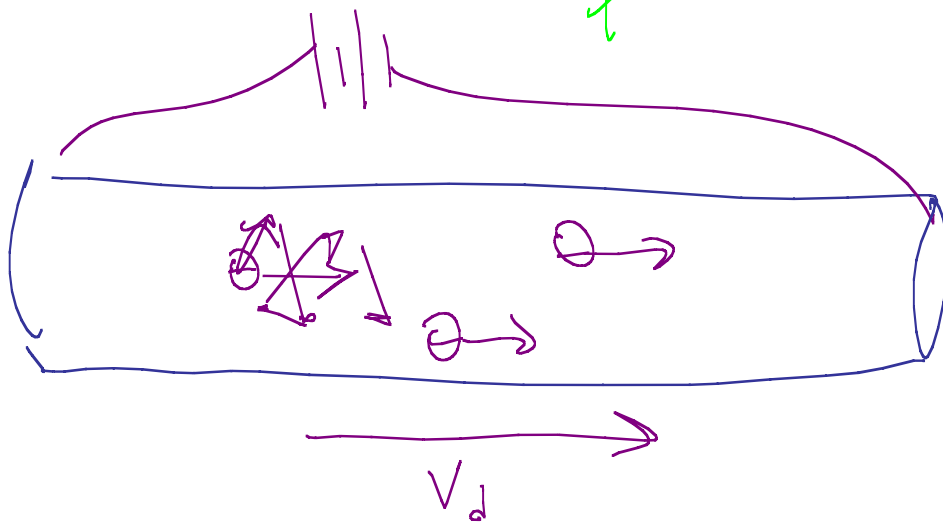

V_d (net vel of electrons)
extremely slow

Snail's pace

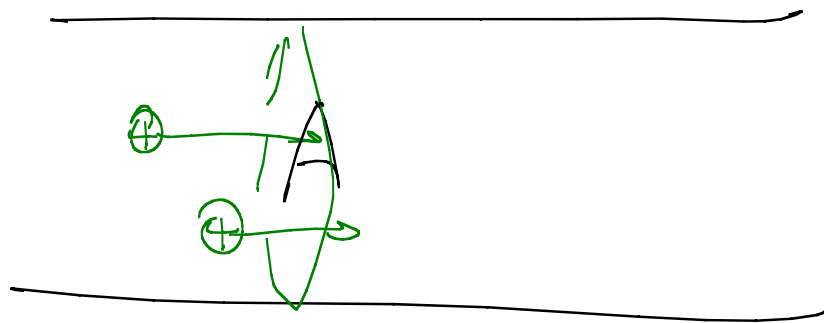

A = x sec area of wire
 q = charge of one charge carrier


Can show

$$I = n A q v_d$$

$\frac{C}{s}$

v_d = drift velocity
 n = number density / volume

Sometimes deal with current density

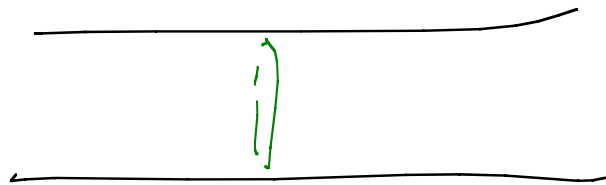

$$J = \frac{I}{A} = n q v_d$$

$\frac{Amp}{m^2}$



Really vectors

$$\vec{J} = nq \vec{v}_d$$

In a real conductor
current is related to
potential difference of
ends of part of conductor

Actually, discuss \vec{E}

$$\vec{J} = \sigma \vec{E}$$

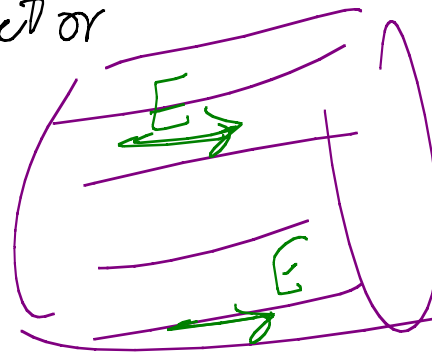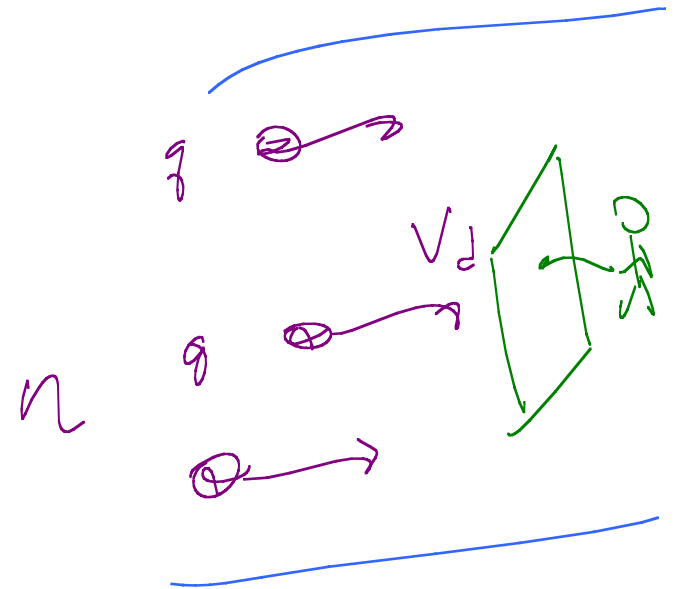

$$J = nq V_d$$