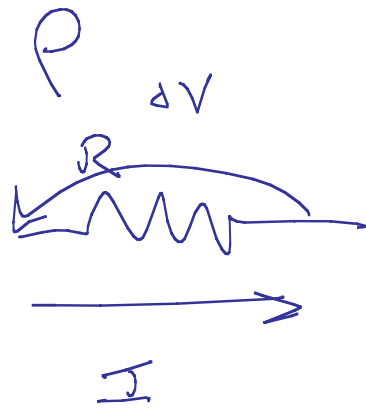


Phys 2120-4 9/26/12

Note Title

9/26/2012

Chap 24 Electric Currents



$$R = \rho \frac{L}{A}$$

Volt


Ohm Ω

$$V = IR$$

Ohm's Law


$$P = VI = I^2 R = \frac{V^2}{R}$$

W




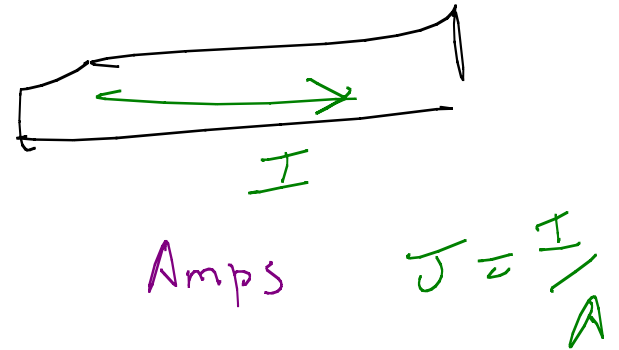




Chp. 25

Electric Circuits

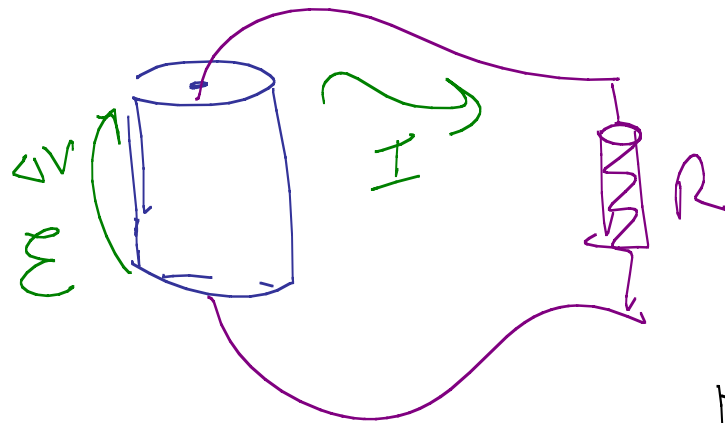


Elements

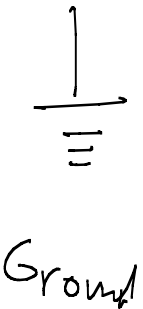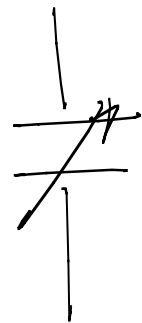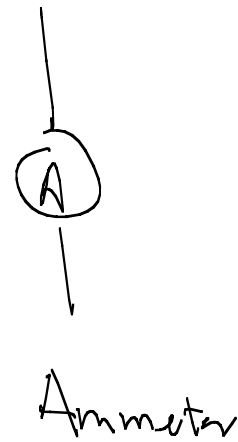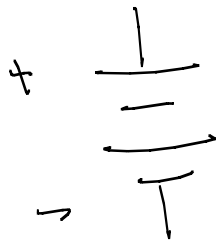

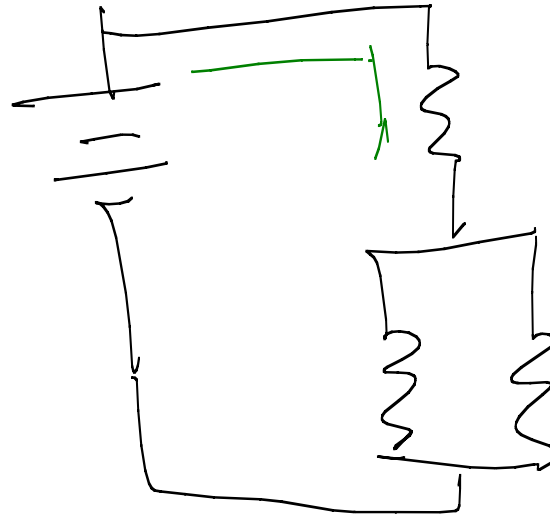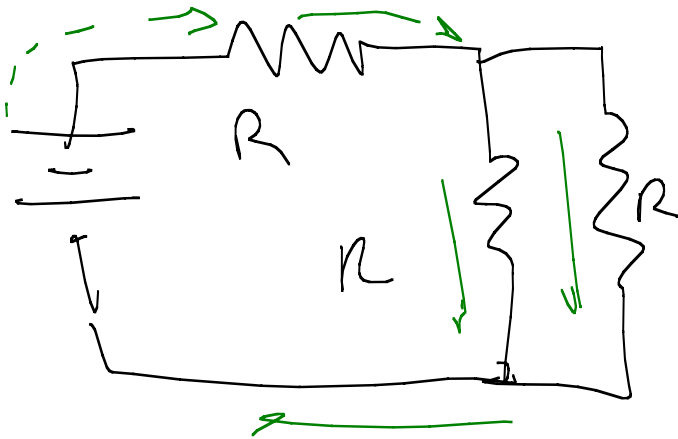

Same

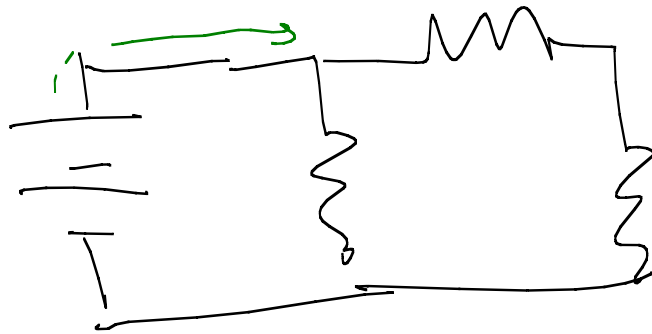

Not the
same

The lengths
of wire are
not important

Series Resistors


Walk around circuit.

List all changes in potential

$$\Rightarrow \Delta V = 0$$

$$\mathcal{E} - IR_1 - IR_2 = 0$$

$$\mathcal{E} = I(R_1 + R_2)$$

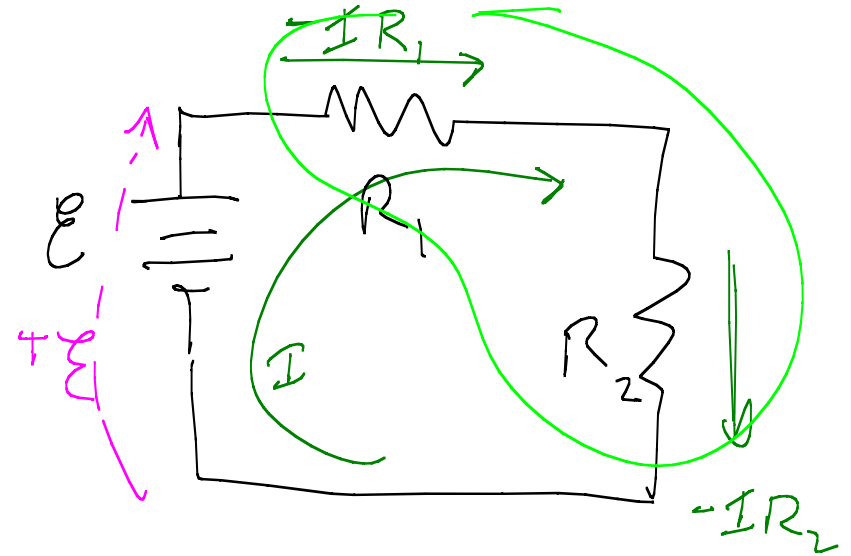


$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

$$\mathcal{E} = IR$$

$$R_{eq} = R_1 + R_2$$


Series Resistors



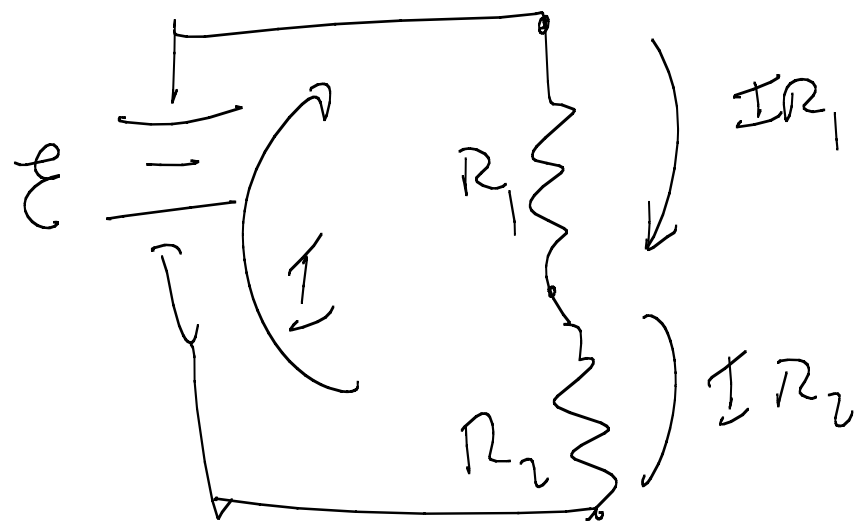

Voltage divider

Internal Resistance of Battery

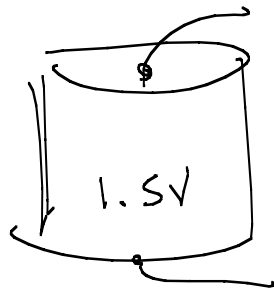

Real battery

$$V_{\text{term}} = \mathcal{E} - I r_{\text{int}}$$

$$\mathcal{E} = (r + R)I$$

